



# *Simulation Tutorial Documentation*



# ***ABOUT VLAB***

- The Virtual Laboratory, represents a pivotal shift in education, as it offers a dynamic and immersive platform for students to explore.
- Traditional physical laboratories, often come with limitations such as accessibility, resource constraints.
- This Virtual Laboratories aims to address these drawbacks by providing a safe, accessible, and flexible environment for hands-on learning, where students can conduct experiments, make mistakes, and learn in an engaging, risk-free setting.
- This underscores the urgent demand for innovative educational tools such as the Virtual Laboratory.



# *ABOUT VLAB*

- Our Trainer Kit is built with the help of Unity.
- We have tried to replicate IC Trainer Kit RS 1001 which is used in DSLD Lab.
- Trainer Kit is integrated with the website using WebGL Build File.



*Lets Get  
Started!!*



# *GET STARTED*




- Click on Trainer Kit.
- Click on Full Screen Mode, to Get Started!!!






# *INITIAL UI*

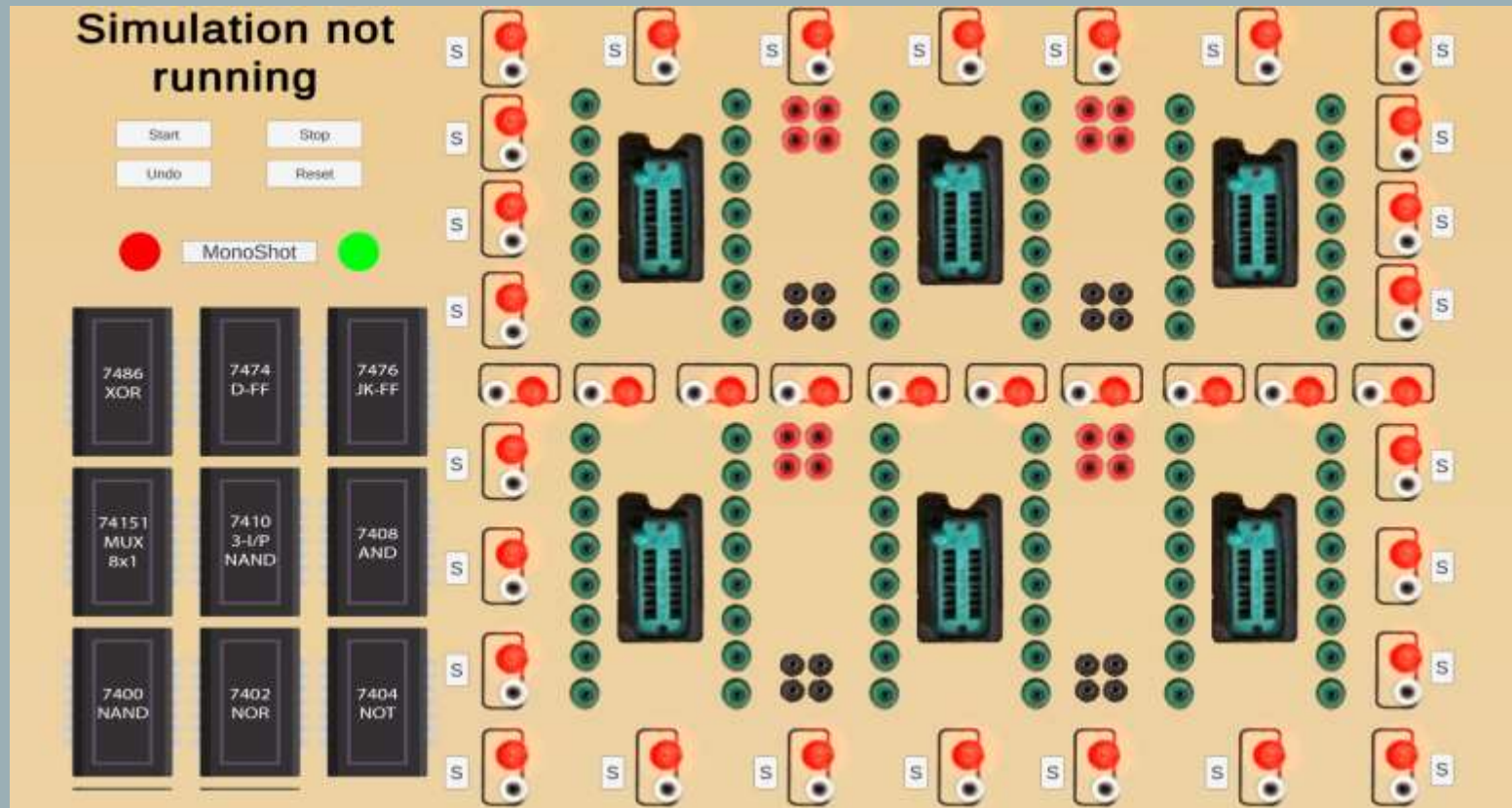

Video Reference - <https://youtu.be/GfxgjZf6VW4>



# ICs

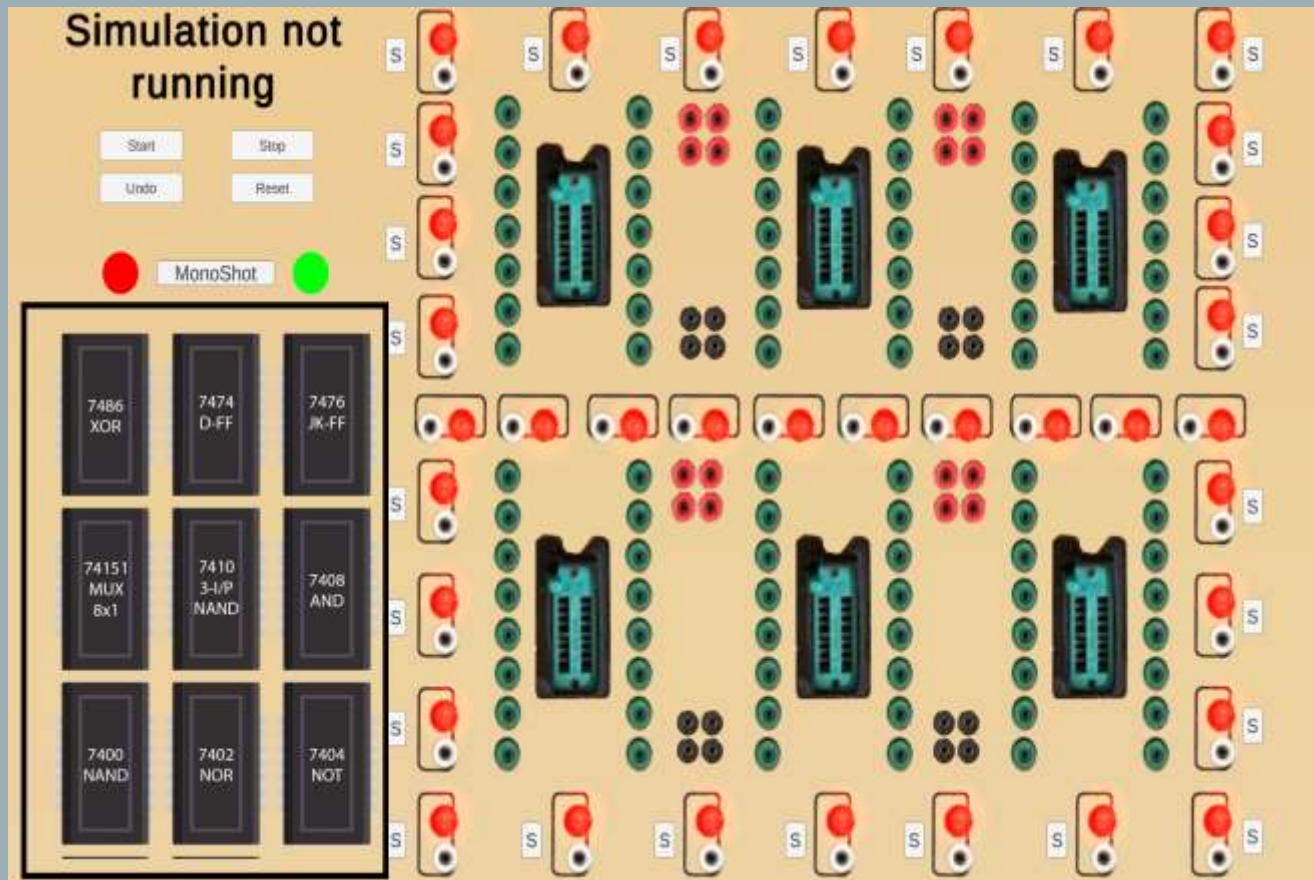


- Left hand side of the Trainer Kit contains the set of ICs.
- Set of ICs we have – AND, OR, NOT, NAND, NOR, XOR, Mod10 Counter and Many more.
- Unleash limitless experimentation with these versatile ICs!






# *SOCKET*

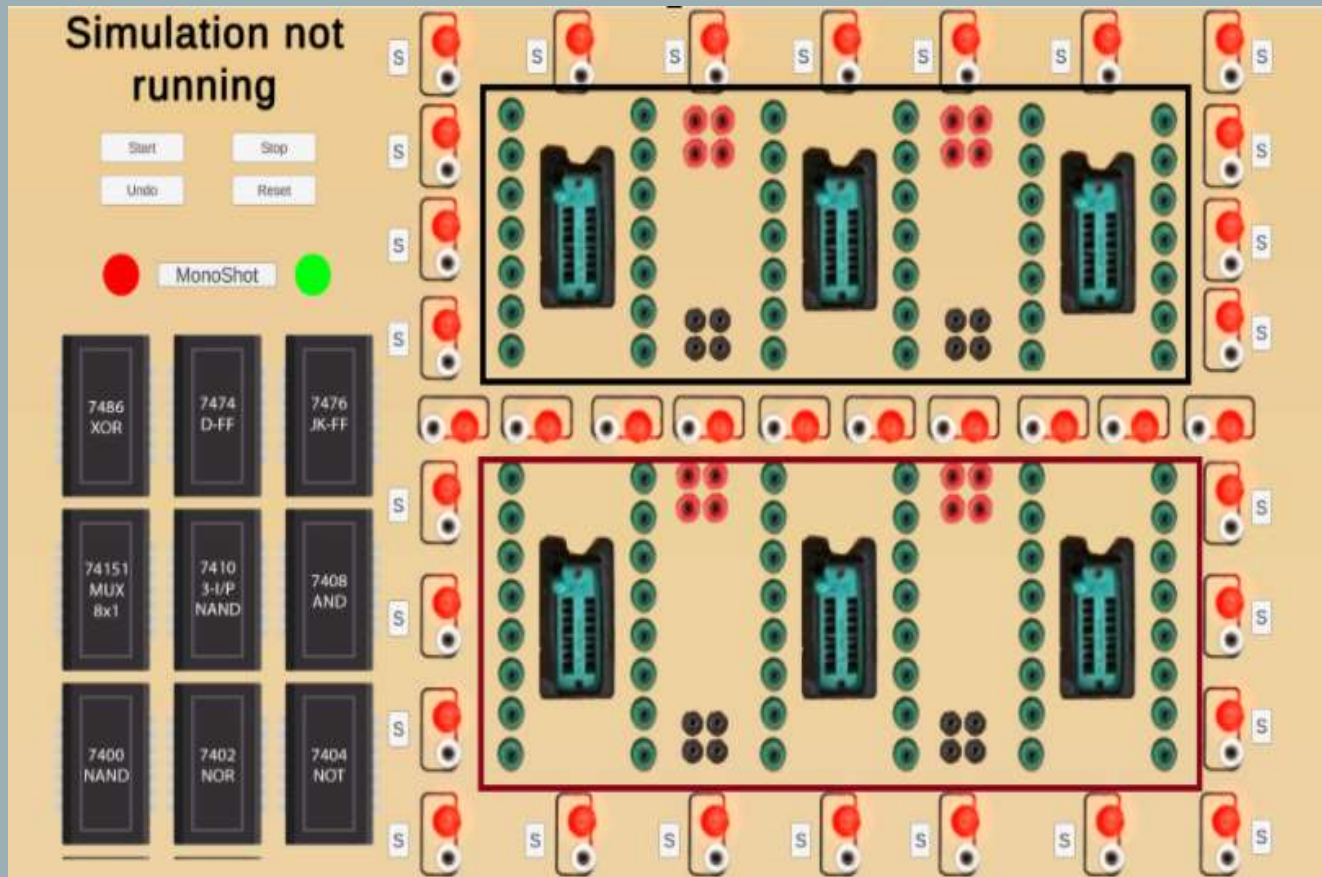

- We have 2 sets of Socket – three 14 pin sockets and three 16 pin socket.
- The Black Box shows 14 Pin Socket.
- The Red Box shows 16 Pin Socket.




# *INPUT AND OUTPUT PINS*

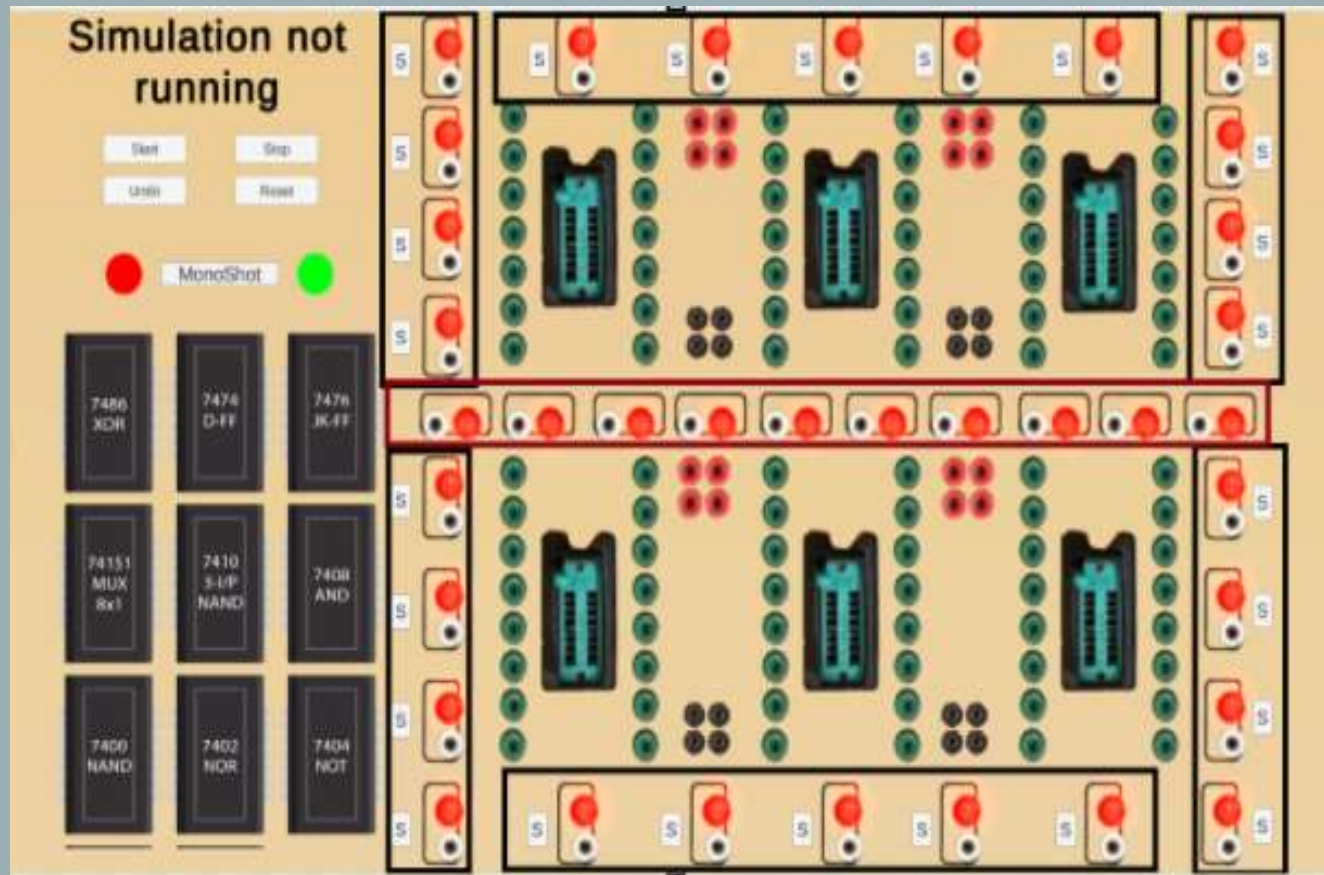

- We have a total of 28 Input Pins and 10 Output Pins.
- Black Box represents set of Input Pins.
- Red Box represents Output Pins.



# *INPUT AND OUTPUT PINS*

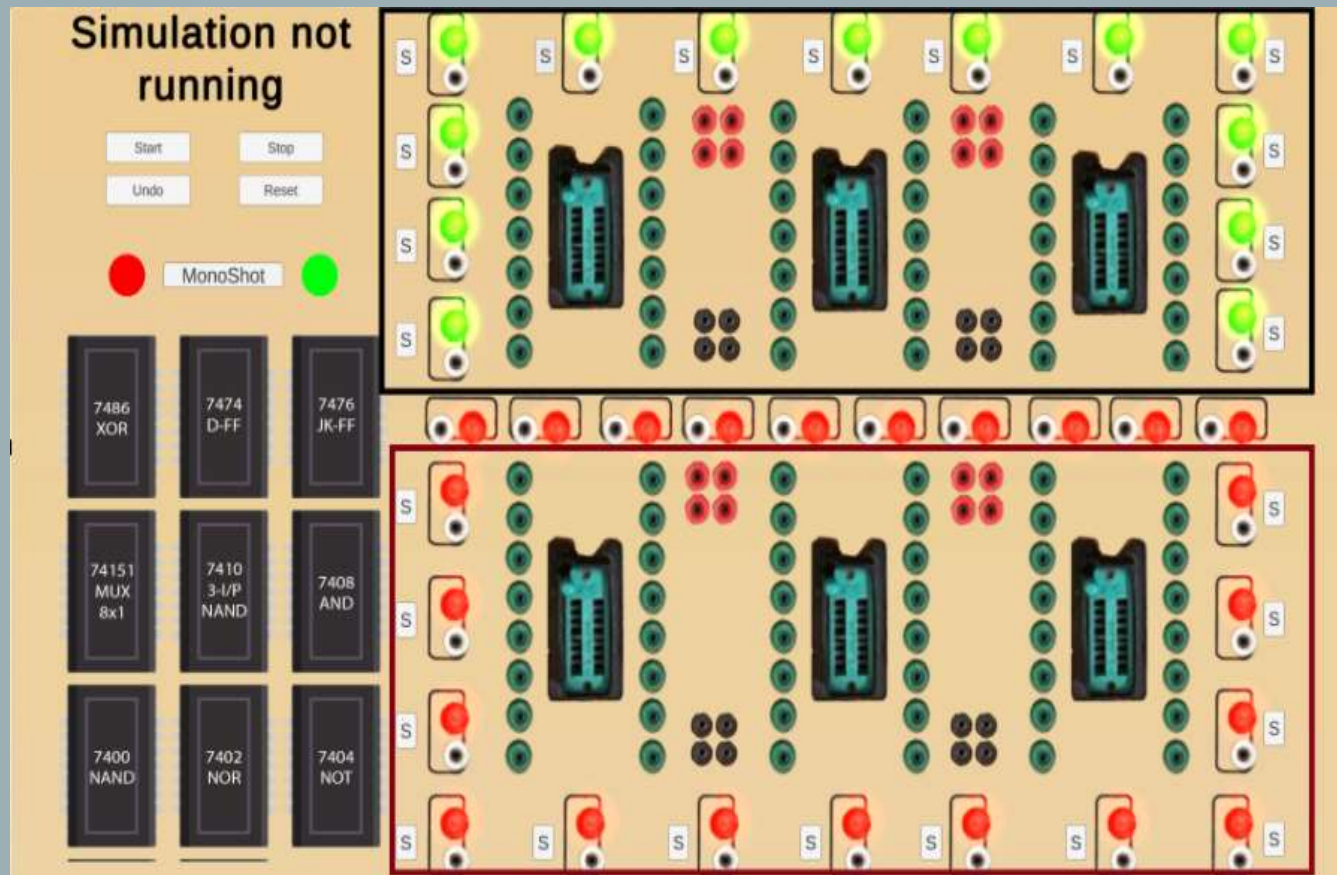


- Click on Switch (S) to toggle between positive and negative input.
- Positive is represented with a Green Light – Black Box.
- Negative is represented with a Red Light – Red Box.






# *Vcc AND GND*

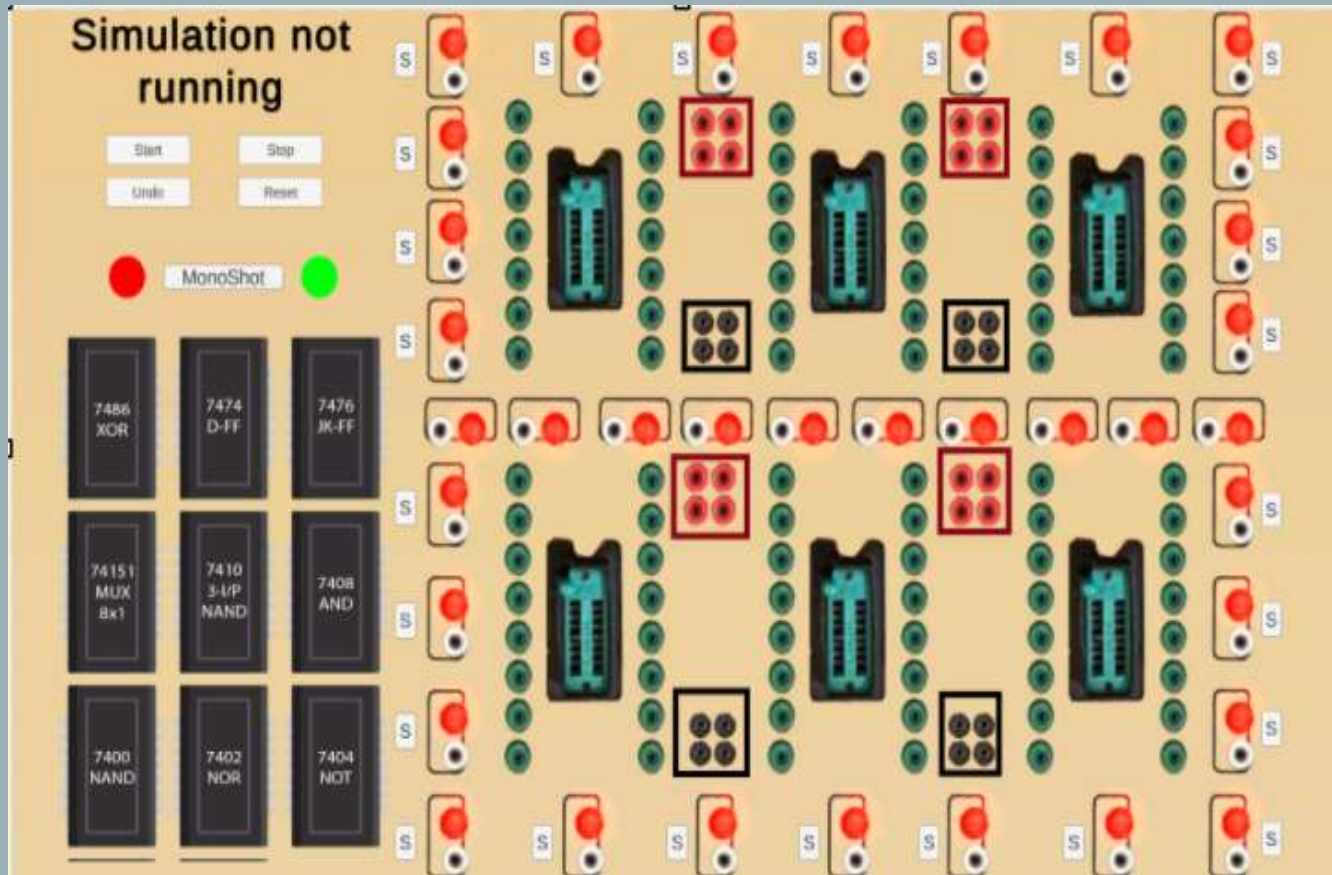

- We have a total of 16 Ground Pins and 16 Vcc Pins.
- Red Box represents Vcc Ports.
- Black Box represents Ground Ports.



# *Simulation Buttons*

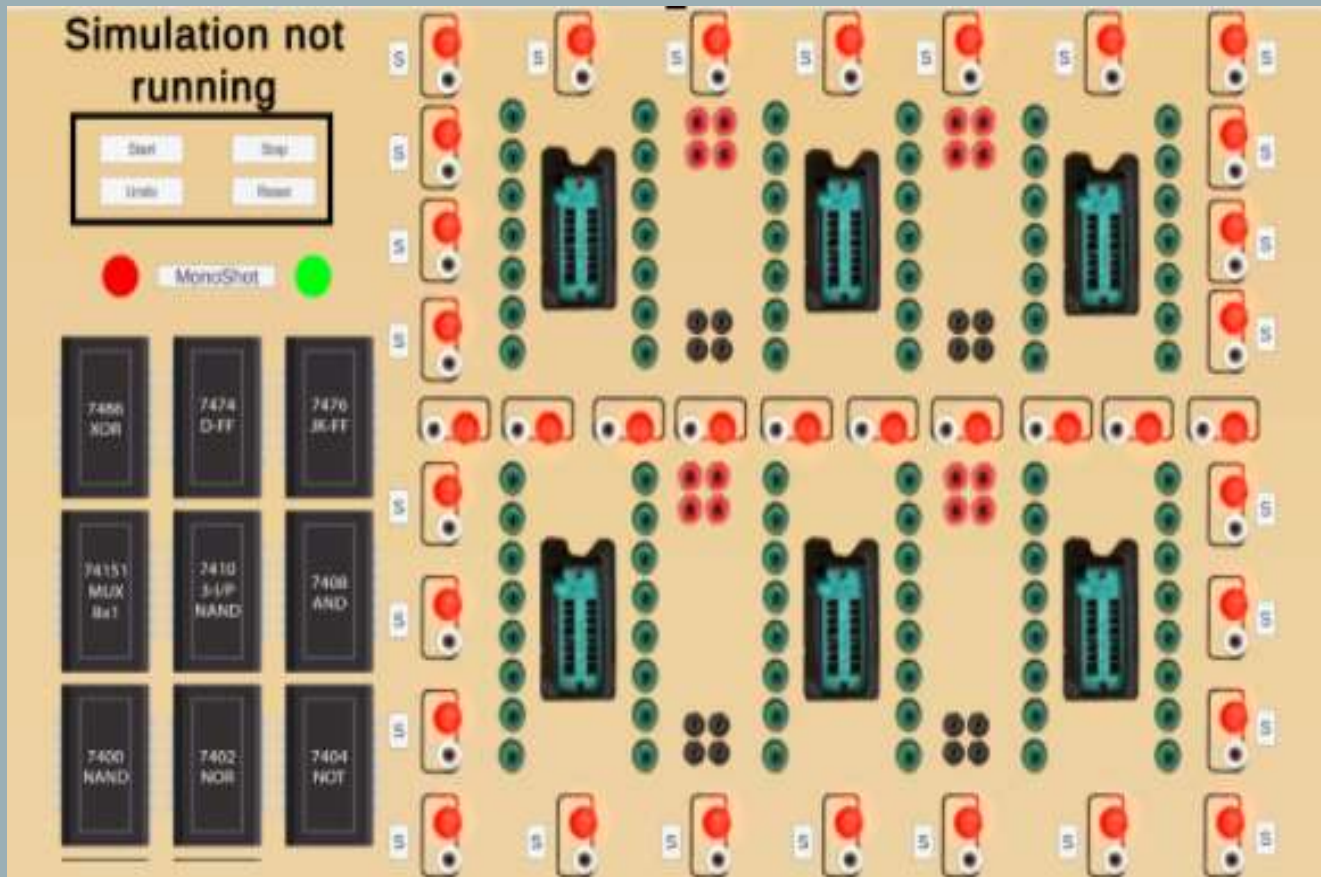


- Start – To Start the Simulation.
- Stop – To Stop the Simulation.
- Reset – To Reset the entire connection made.
- Undo – To undo the conditions to go back.






# *Simulation Status*

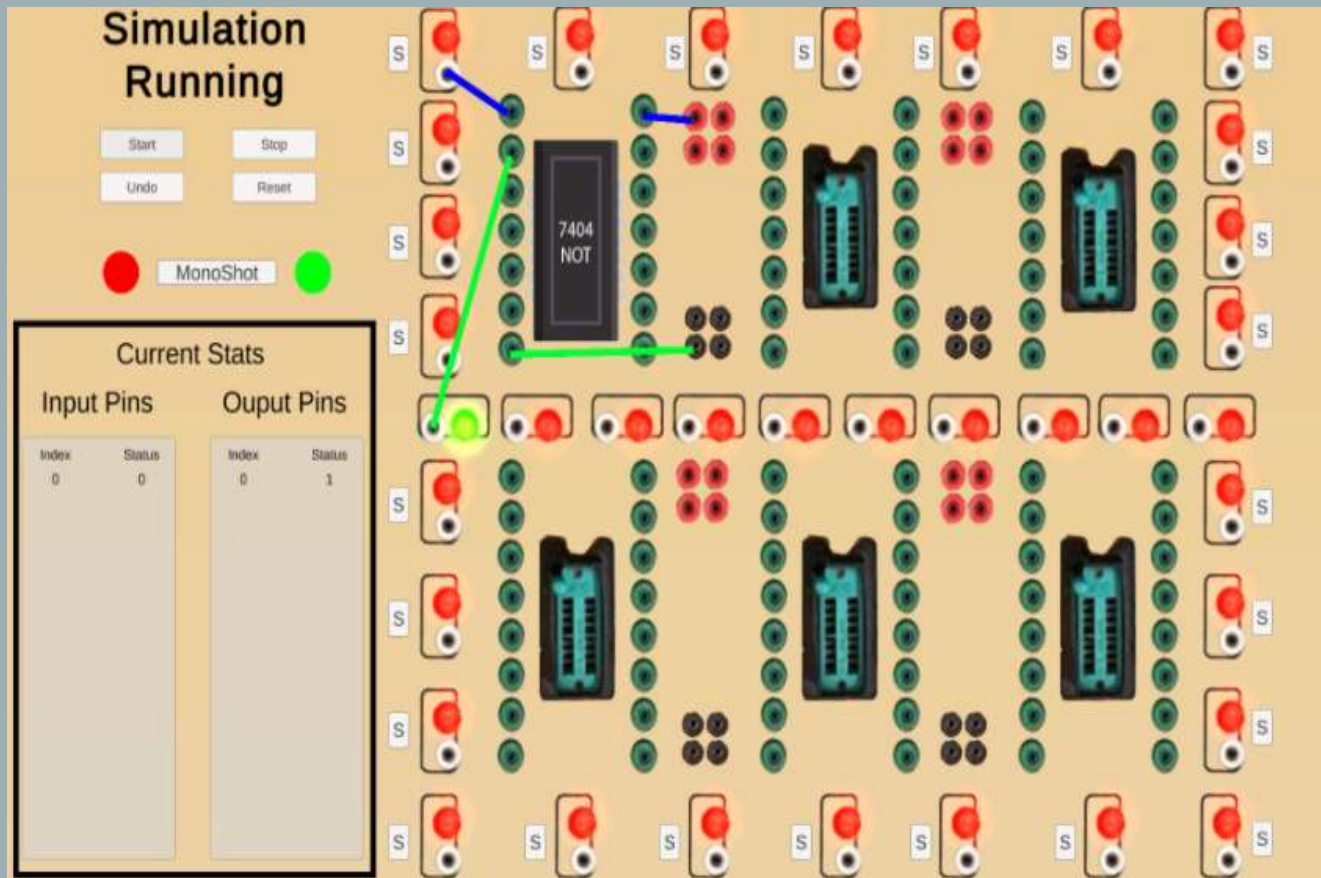

- Drag and Drop IC to start the simulation.
- When you start the simulation, the Black Box represents the Simulation Status.
- Input Pins and Output Pins give corresponding Status of the current connection.



# *Clock - Monoshot*

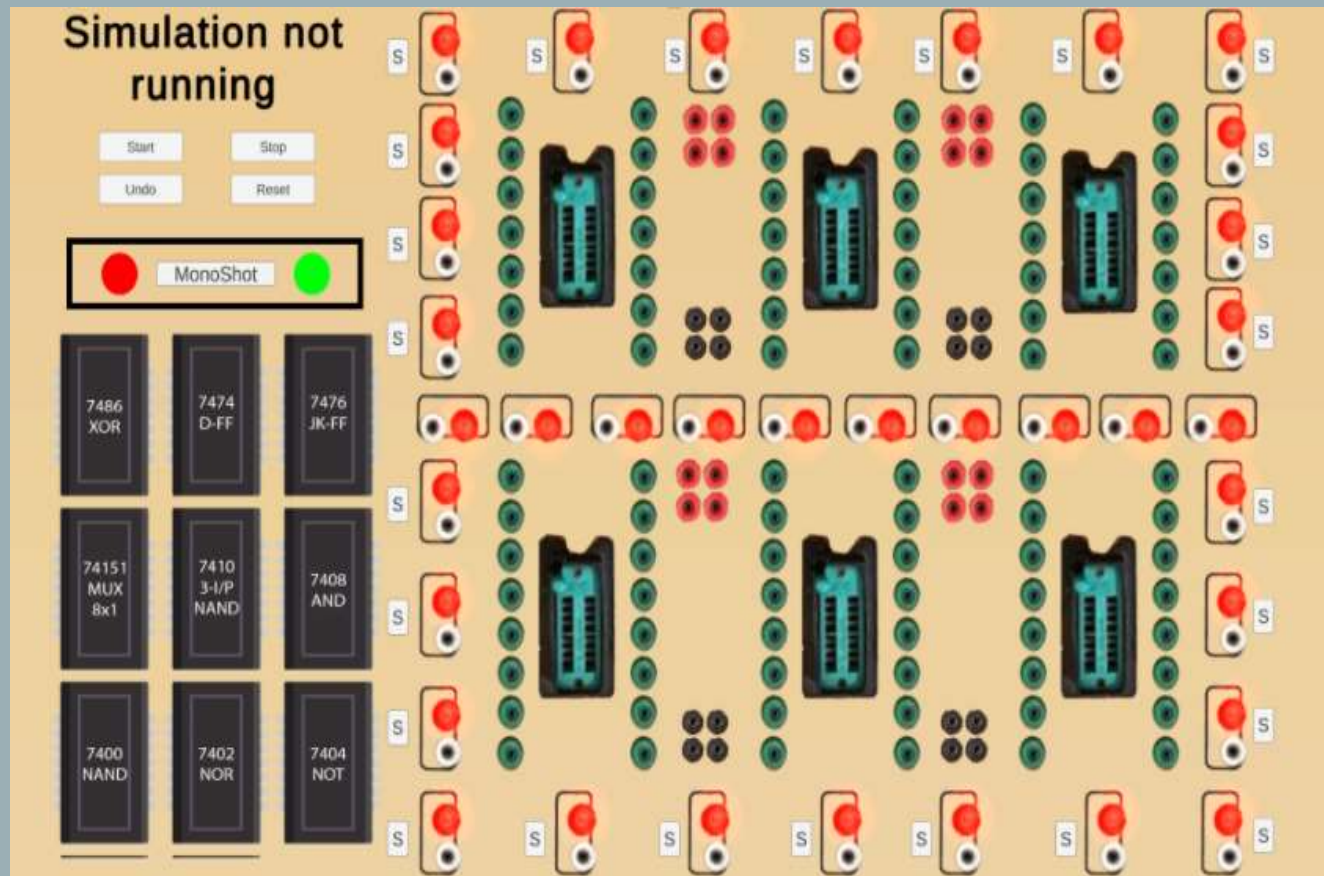

- Monoshot represents clock pulse.
- Click on Monoshot, for each clock pulse.
- Green represents positive clock pulse.
- Red represents negative clock pulse.




# ***BASIC GATES***

- Basic gates are fundamental building blocks of digital circuits.
- NOT gate (IC 7404): Outputs the opposite of its input.
- AND gate (IC 7408): Outputs true only when all inputs are true.
- OR gate (IC 7432): Outputs true when at least one input is true.

# ***BASIC GATE – NOT GATE (IC 7404)***



**Truth Table**

A (Input)	$Y = \bar{A}$ (Output)
0	1
1	0

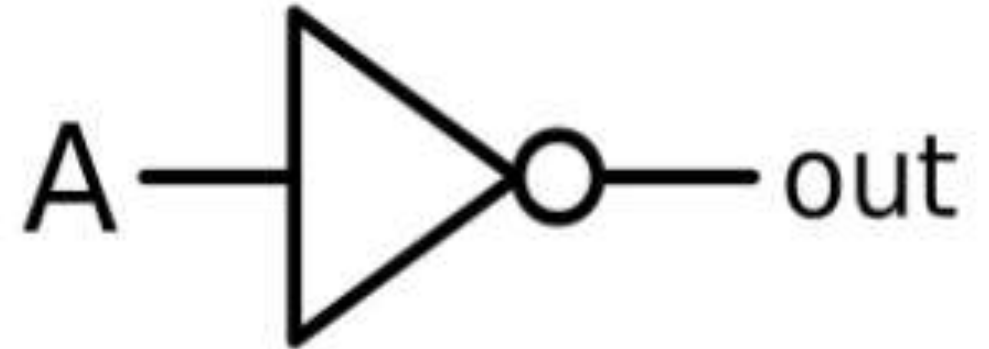



# *BASIC GATE – NOT GATE (IC 7404)*

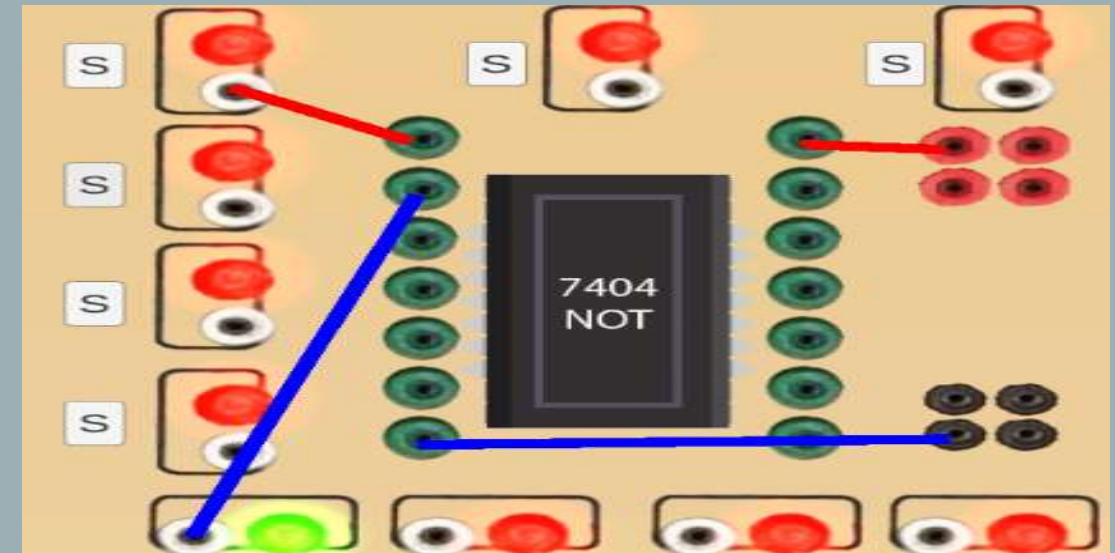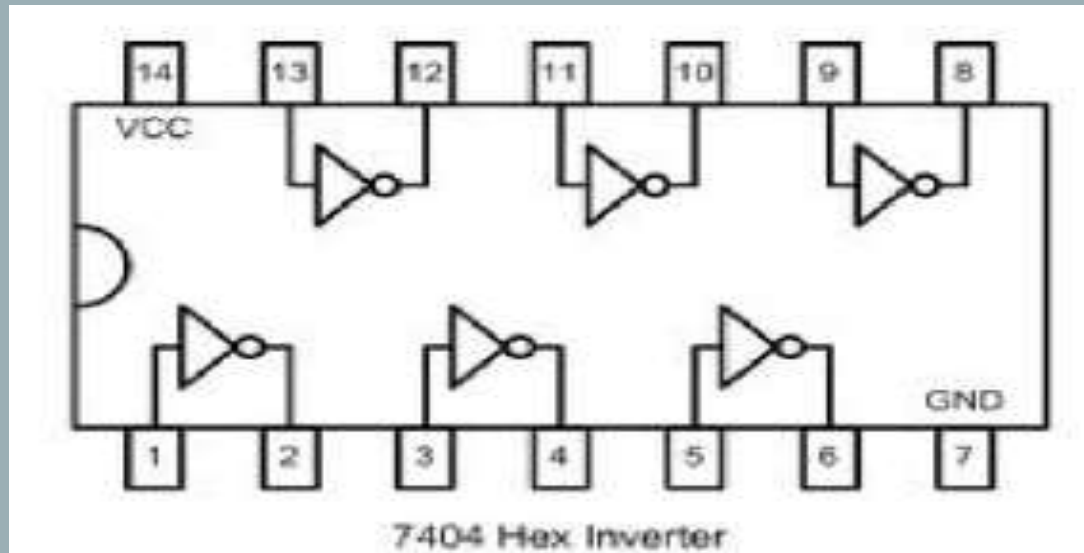


Video Reference - [https://youtu.be/3WC\\_gcgBTHg](https://youtu.be/3WC_gcgBTHg)



# *BASIC GATE – AND GATE (IC 7408)*

Truth Table

A (Input 1)	B (Input 2)	X = (A.B)
0	0	0
0	1	0
1	0	0
1	1	1

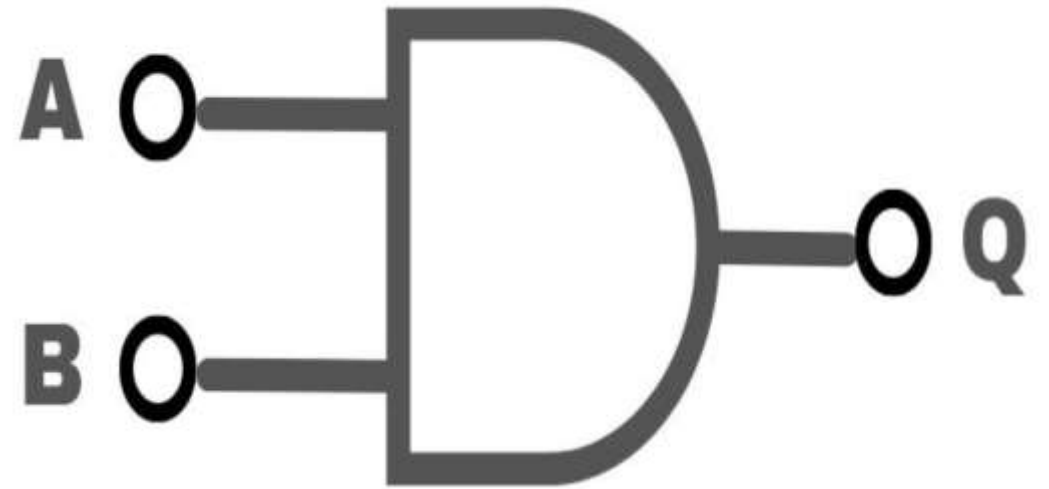

# *BASIC GATE – AND GATE (IC 7408)*

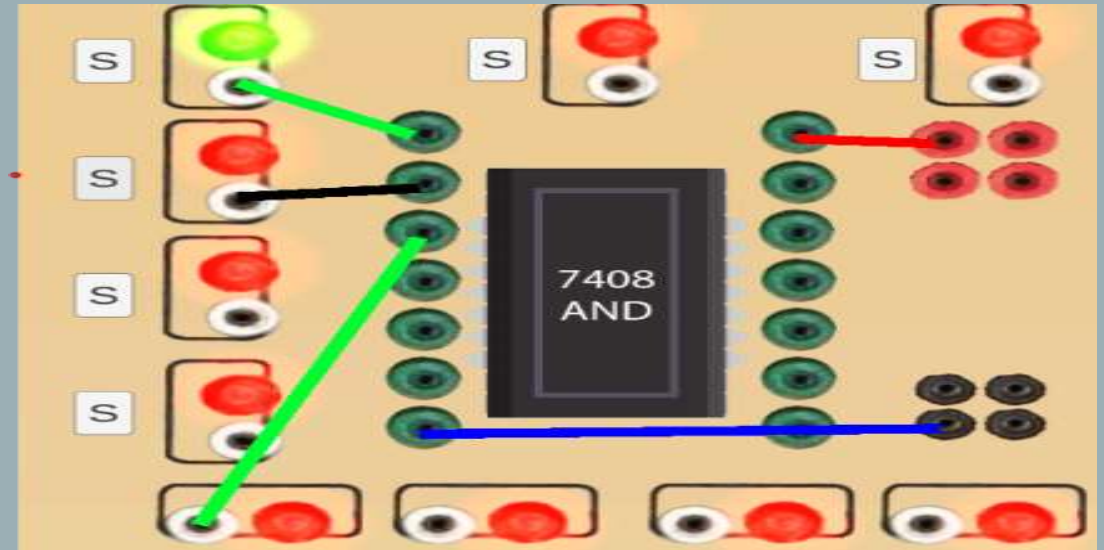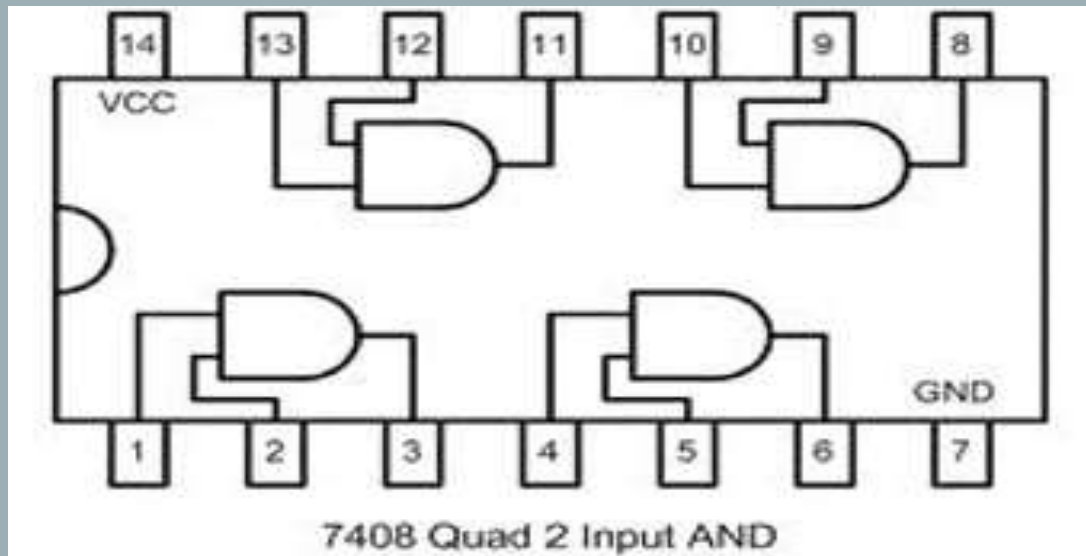

Video Reference - [https://youtu.be/3WC\\_gcgBTHg](https://youtu.be/3WC_gcgBTHg)

# ***BASIC GATE – OR GATE (IC 7432)***



Truth Table

Input A	Input B	Output
0	0	0
0	1	1
1	0	1
1	1	1





# *BASIC GATE – OR GATE (IC 7432)*

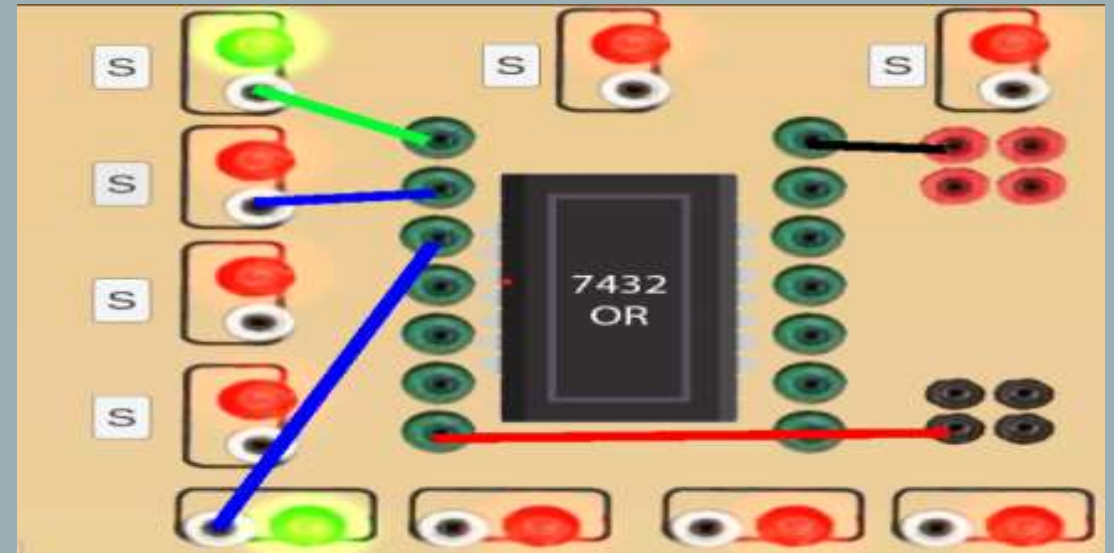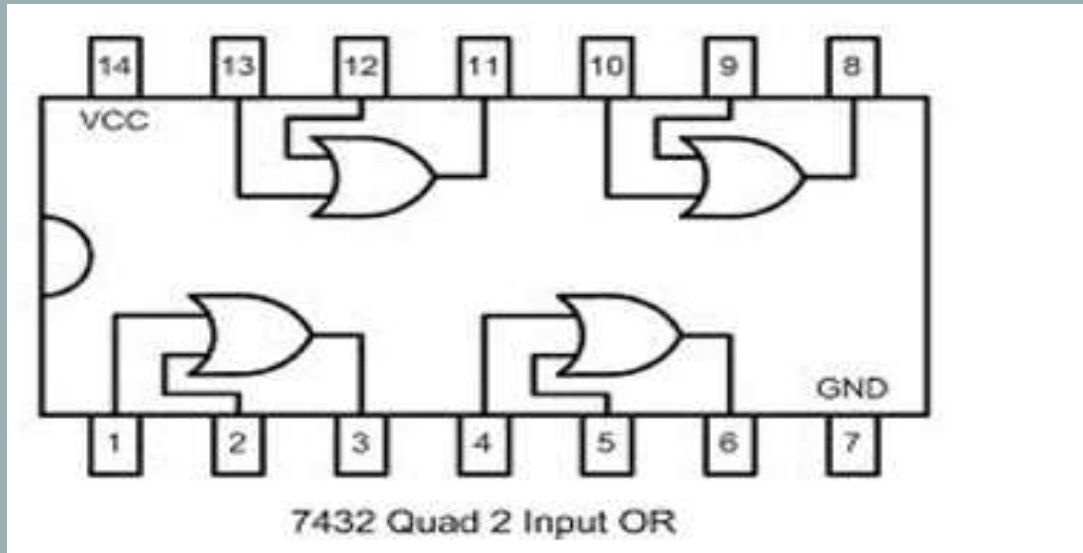


Video Reference - [https://youtu.be/3WC\\_gcgBTHg](https://youtu.be/3WC_gcgBTHg)



# ***XOR GATE (IC 7486)***

**Truth Table**

A (Input 1)	B (Input 2)	$X = A'B + AB'$
0	0	0
0	1	1
1	0	1
1	1	0

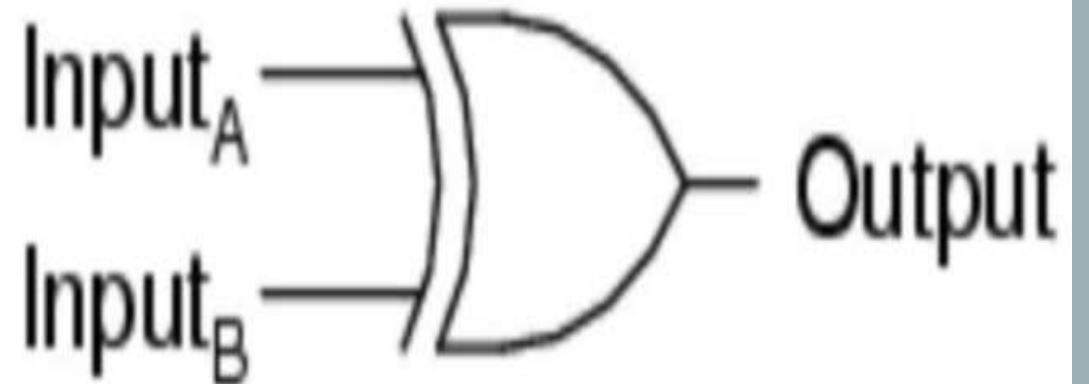

# *XOR GATE (IC 7486)*

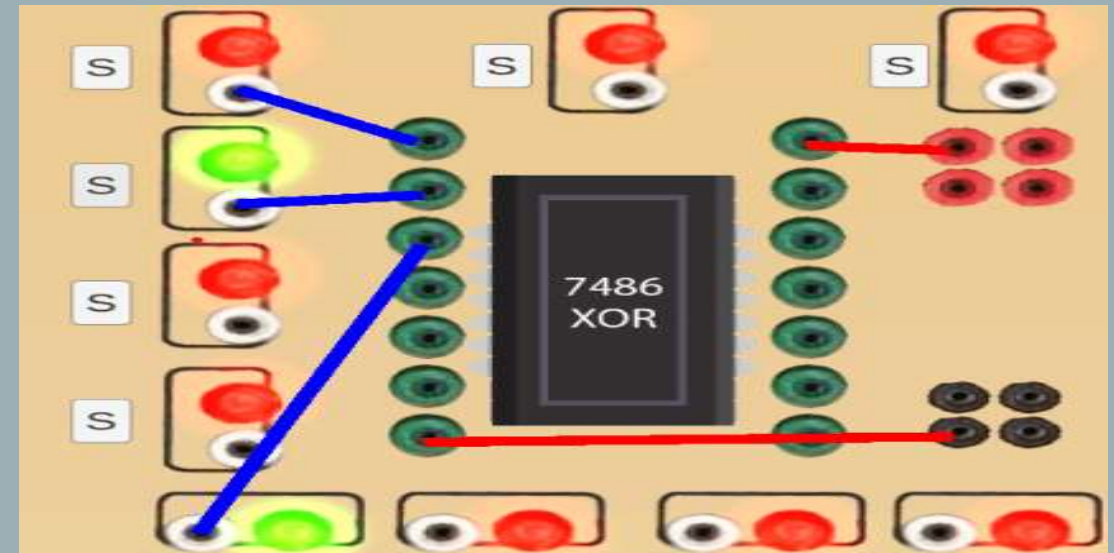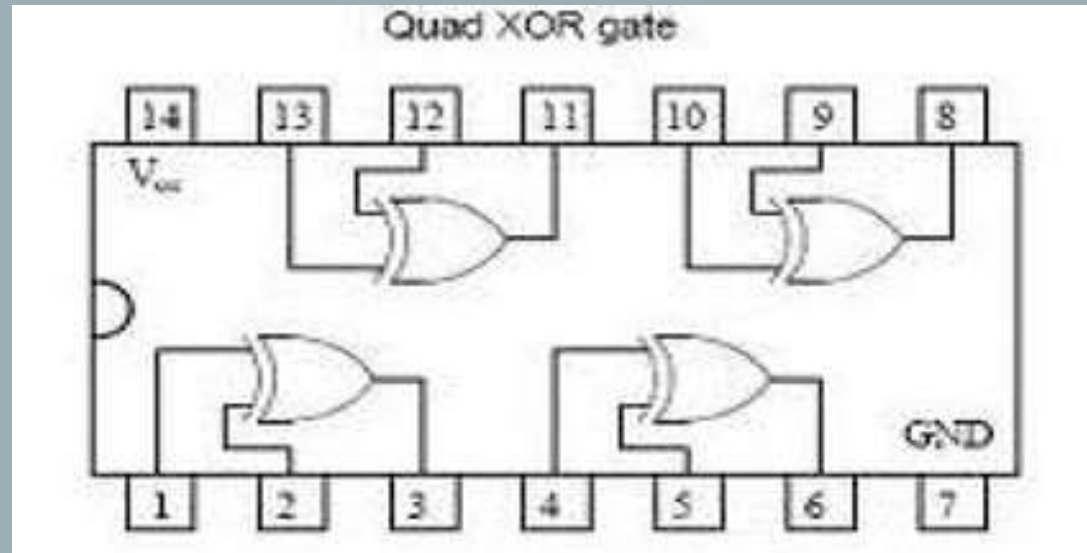



# *UNIVERSAL GATES*

- Universal gates can be used to implement any other logic gate.
- NAND gate (IC 7400): Can implement AND, OR, and NOT functions.
- NOR gate (IC 7402): Can implement AND, OR, and NOT functions.








# *UNIVERSAL GATE – NAND GATE (IC 7400)*

Truth Table

Input A	Input B	$X = (A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

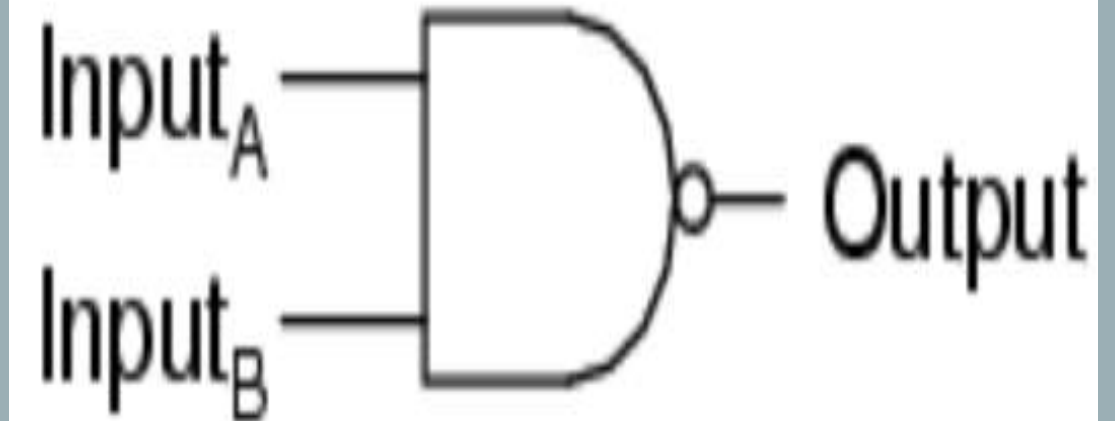

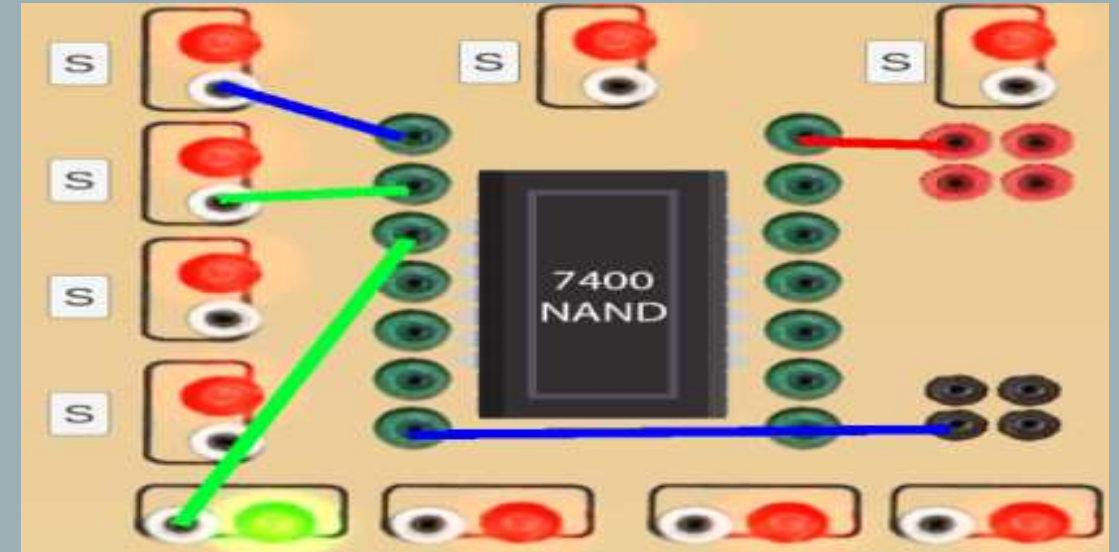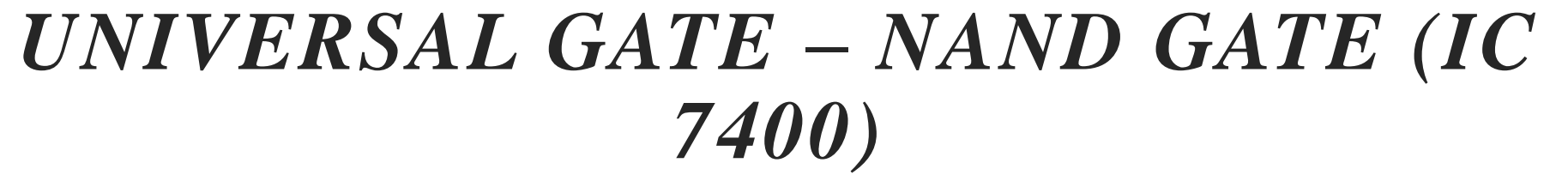


26



# *UNIVERSAL GATE – NOR GATE (IC 7402)*

**Truth Table**

Input A	Input B	$0 = (A + B)'$
0	0	1
0	1	0
1	0	0
1	1	0

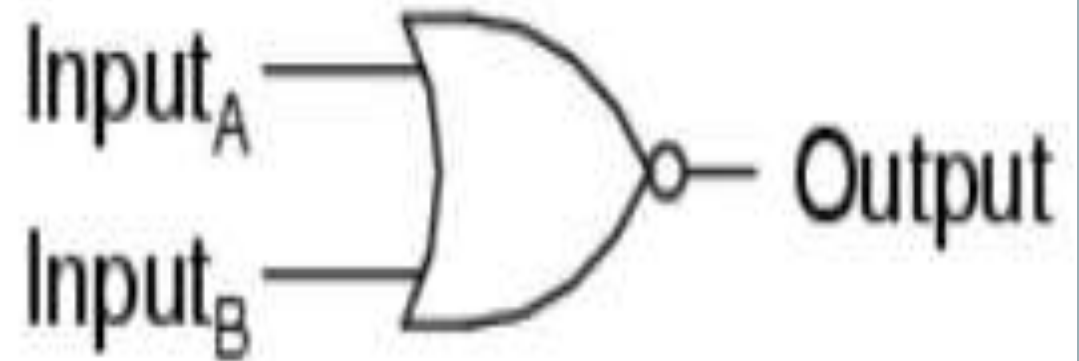

# UNIVERSAL GATE – NOR GATE (IC 7402)

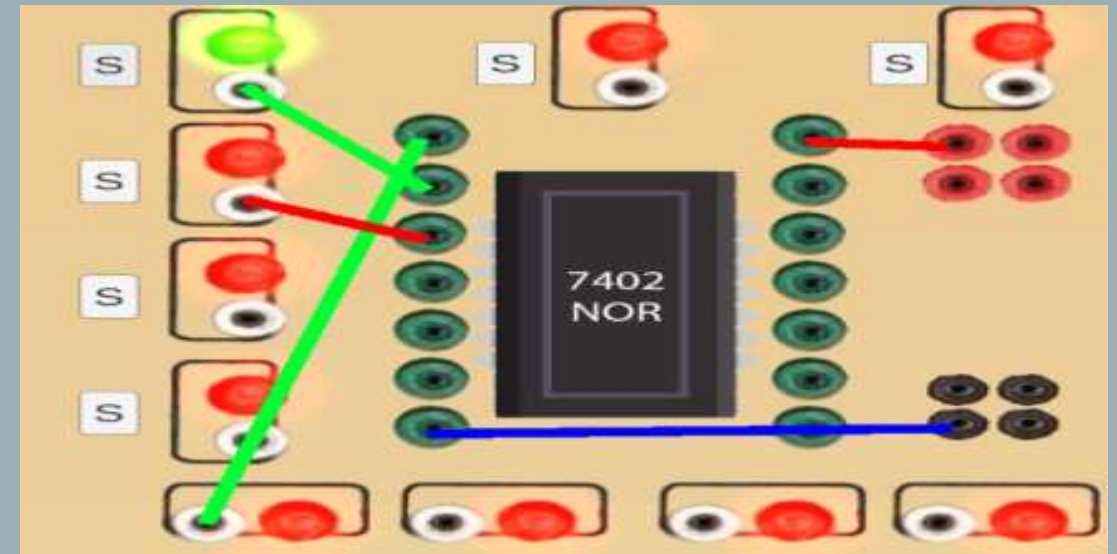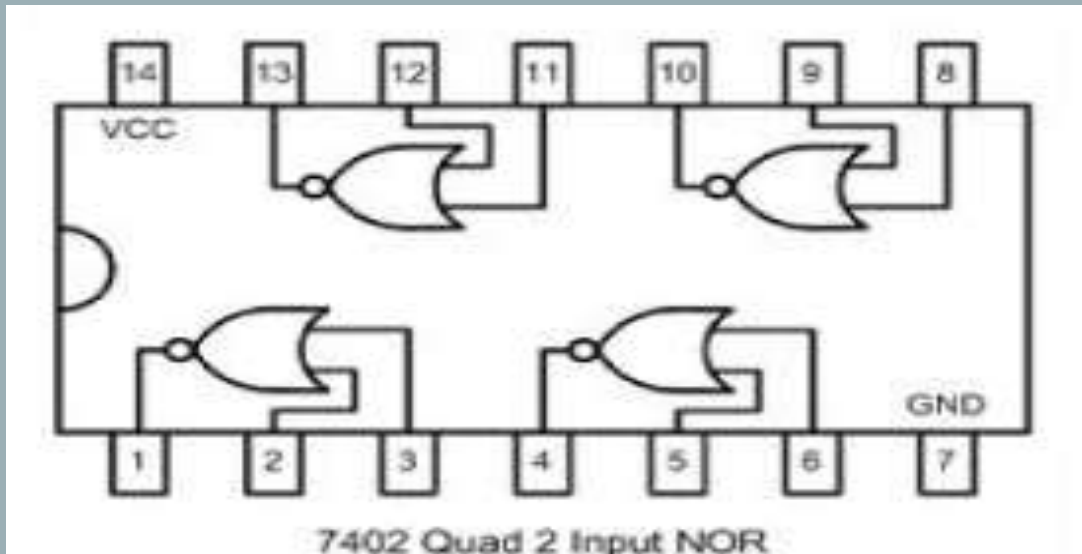

Video Reference - <https://youtu.be/G1lWlpj-Bayg>






# ***ADDER SUBTRACTOR CIRCUIT***


- An adder-subtractor circuit performs both addition and subtraction operations on binary numbers.
- Full adder: Adds three binary inputs and produces a sum and carry output.
- Half subtractor: Subtracts two binary inputs and produces a difference and borrow output.

# ***FULL ADDER***

A	B	C <sub>in</sub>	SUM (S)	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

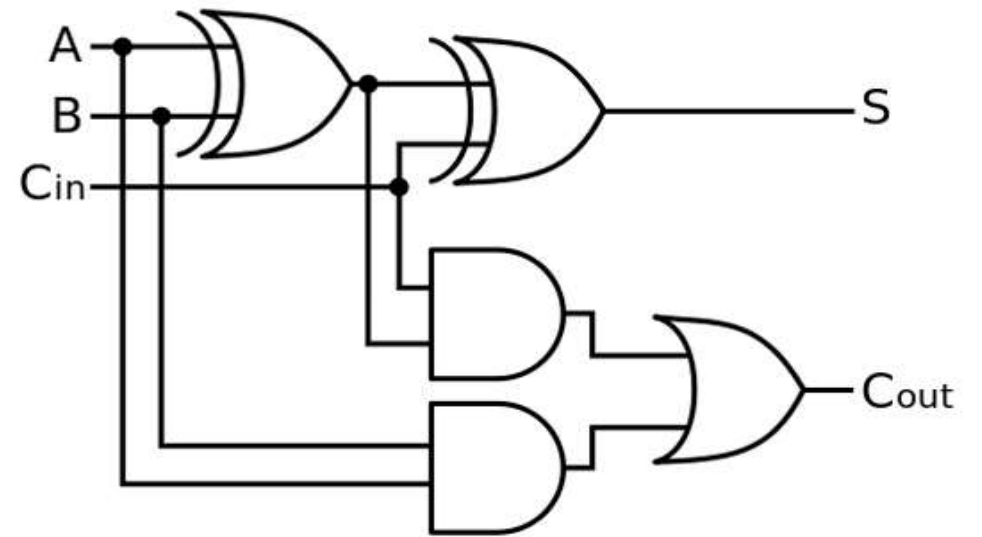

# ***FULL ADDER***

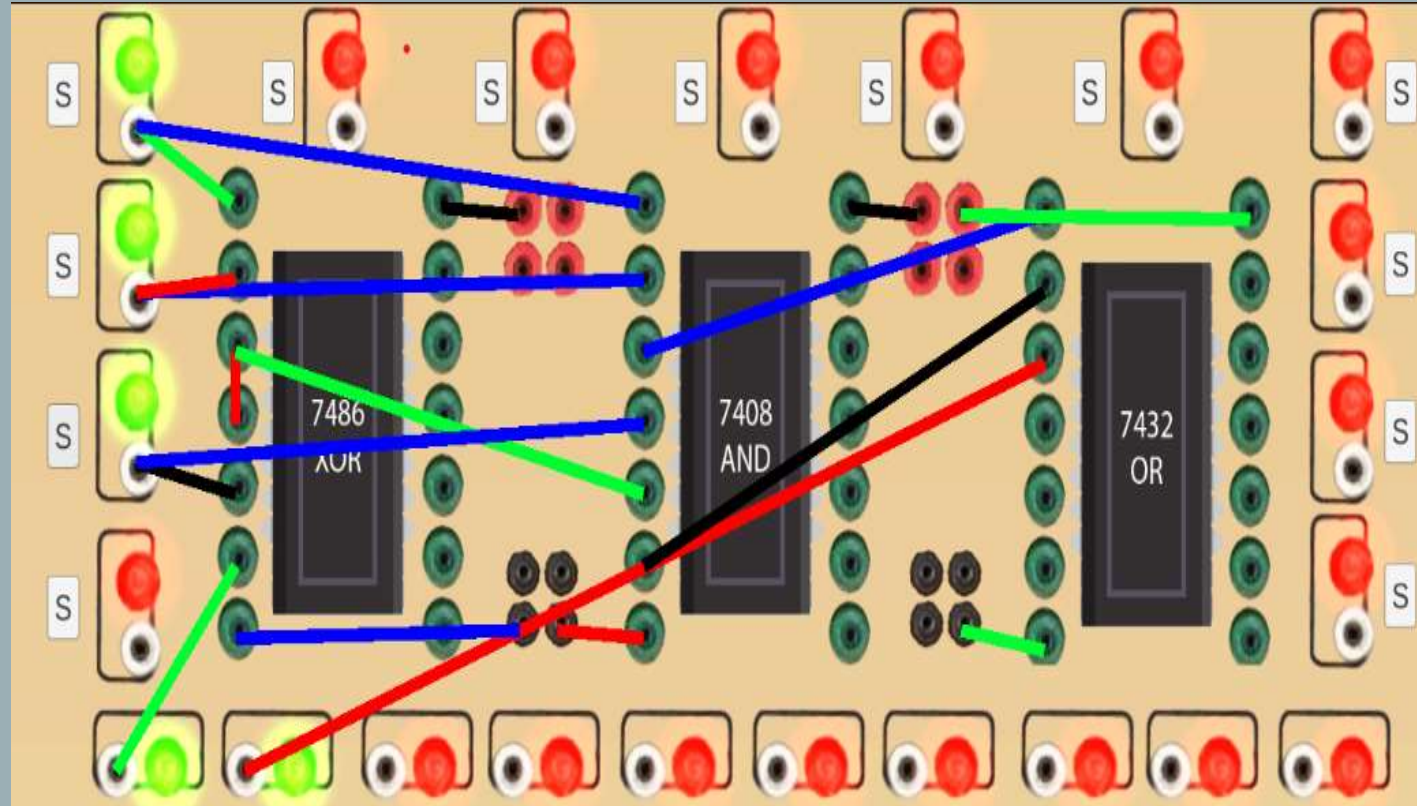


Video Reference - <https://youtu.be/jCh8tFqPx9k>

# *HALF SUBTRACTOR*


A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Truth Table

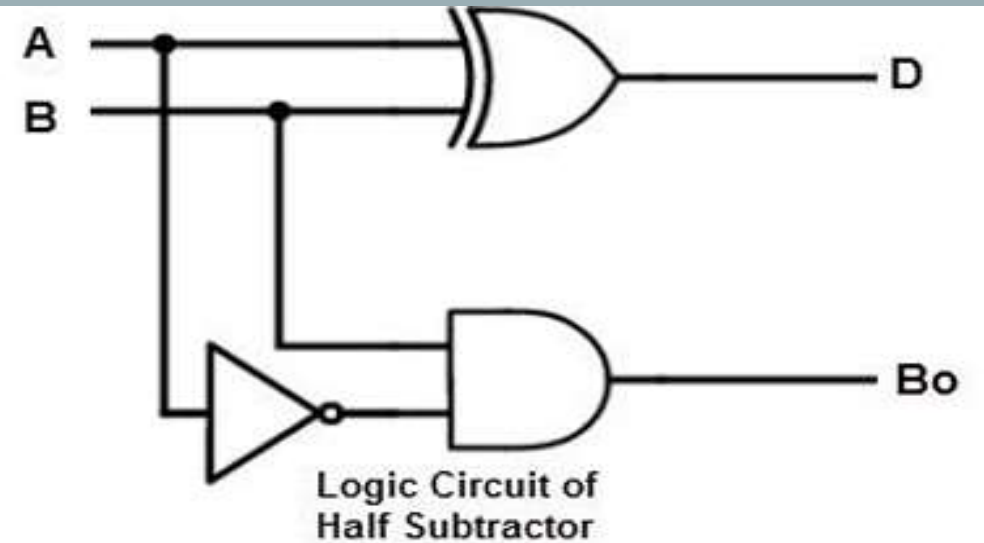



# *HALF SUBTRACTOR*

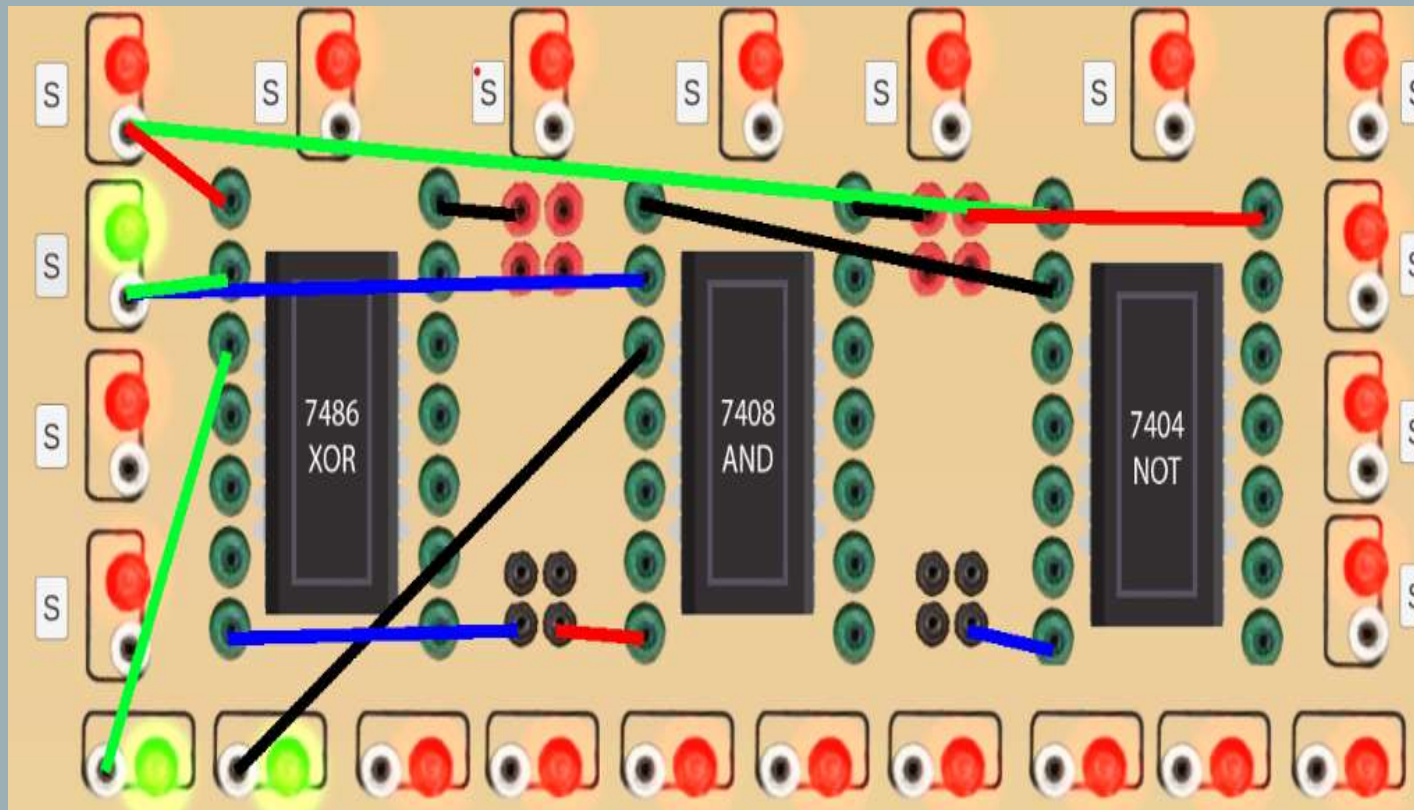

Video Reference - <https://youtu.be/jCh8tFqPx9k>




# ***CODE CONVERTER AND MAGNITUDE COMPARATOR CIRCUIT***


- A code converter circuit transforms one digital code to another, such as binary to BCD or Gray code.
- A magnitude comparator circuit compares the relative magnitudes of two binary numbers and produces output indicating their relationship (greater than, less than, or equal).
- The Excess-3code for a decimal digit is the binary combination corresponding to the decimal digit plus 3.

# MAGNITUDE COMPARATOR

A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

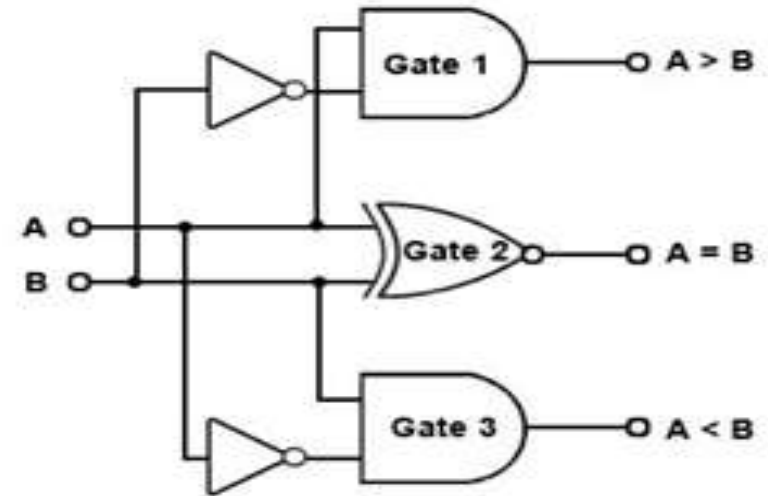

# *MAGNITUDE COMPARATOR*

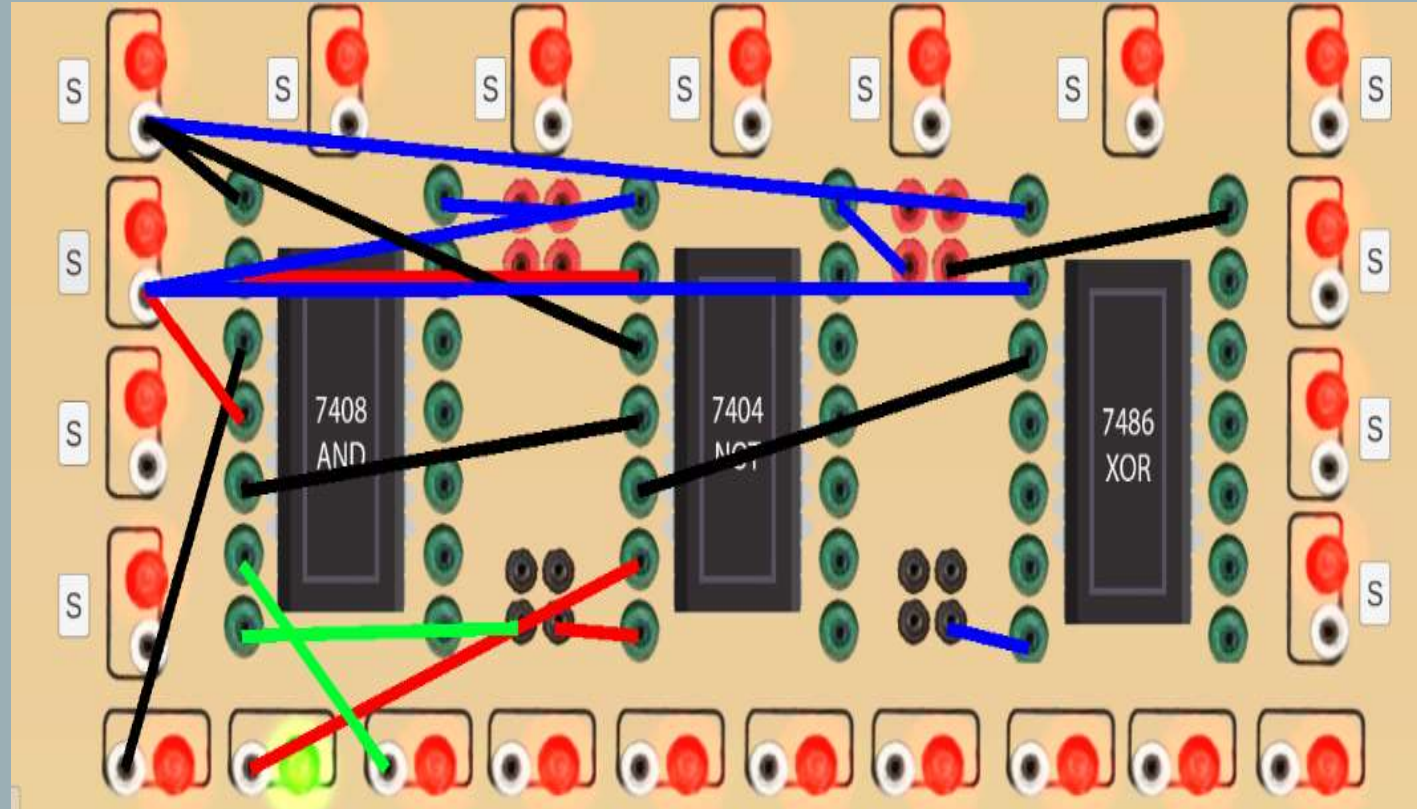

Video Reference - <https://youtu.be/HUaKC1RYCxY>






# *DATA PROCESSING CIRCUIT*

- A data processing circuit manipulates digital data according to specified operations, such as addition, subtraction, or logical functions.
- An 8:1 multiplexer selects one of eight input data sources and forwards it to a single output based on control signals.





# *DATA PROCESSING CIRCUIT – 8:1 MUX – IC 74151*

Select Lines			Output
S2	S1	S0	Out
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

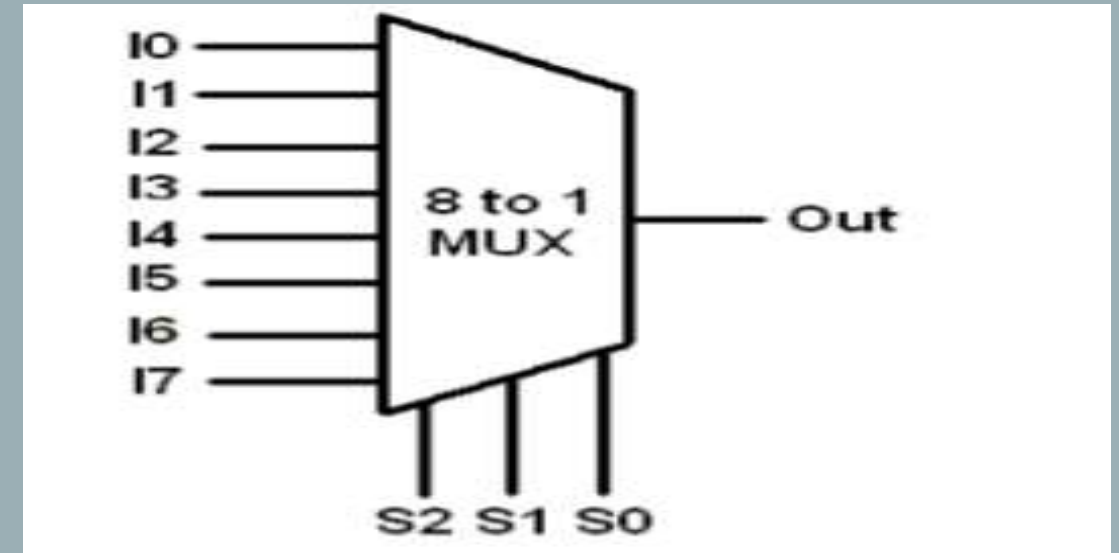
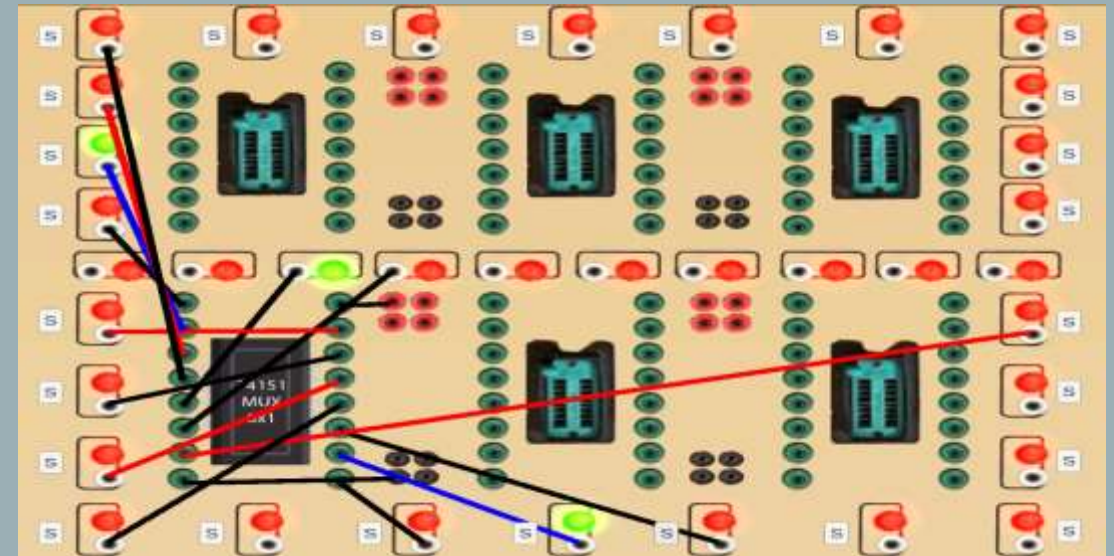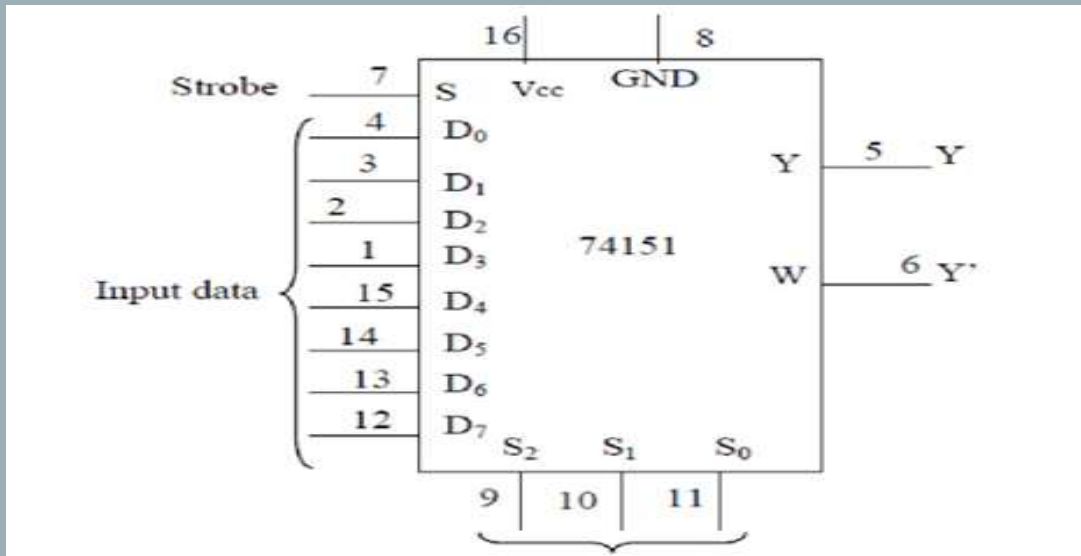
# *DATA PROCESSING CIRCUIT – 8:1 MUX – IC 74151*



Video Reference - <https://youtu.be/QohxwFDptnI>




# ***FLIP FLOP – SR FLIP FLOP AND D FLIP FLOP***

- Flip-flops are digital circuits capable of storing binary states, used as memory elements in sequential logic circuits.
- A SR flip-flop stores one bit of data and has two inputs: Set (S) and Reset (R), which toggle its output.
- A D flip-flop, or data flip-flop, stores one bit of data and has a single input (D) that sets its state when the clock input transitions.




# *FLIP FLOP – SR FLIP FLOP*

S	R	Q	Q+
1	1	0	0
1	1	1	1
0	1	X	0
1	0	X	1
0	0	X	1

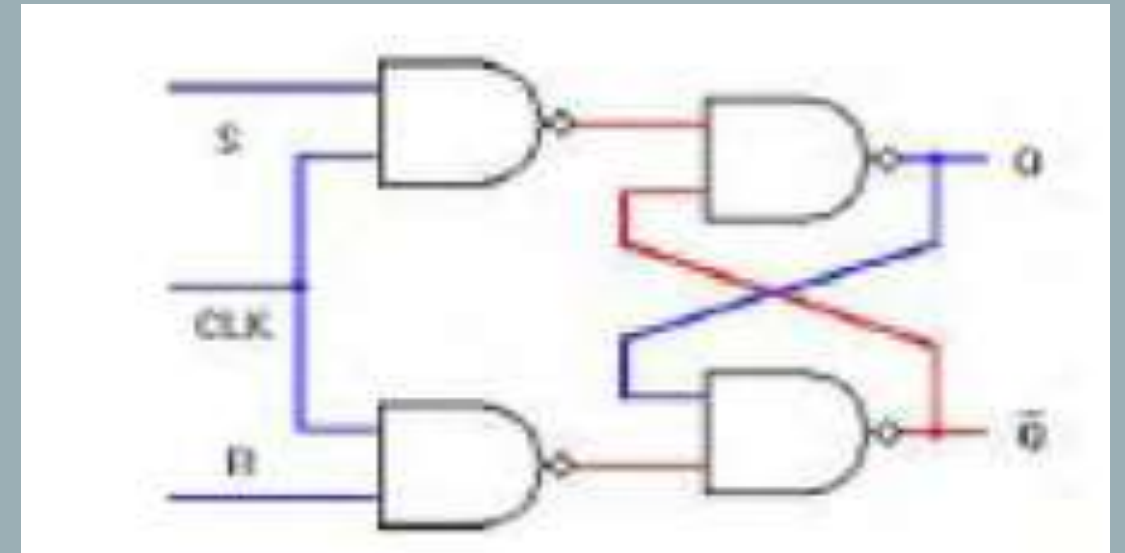


# *FLIP FLOP – SR FLIP FLOP*

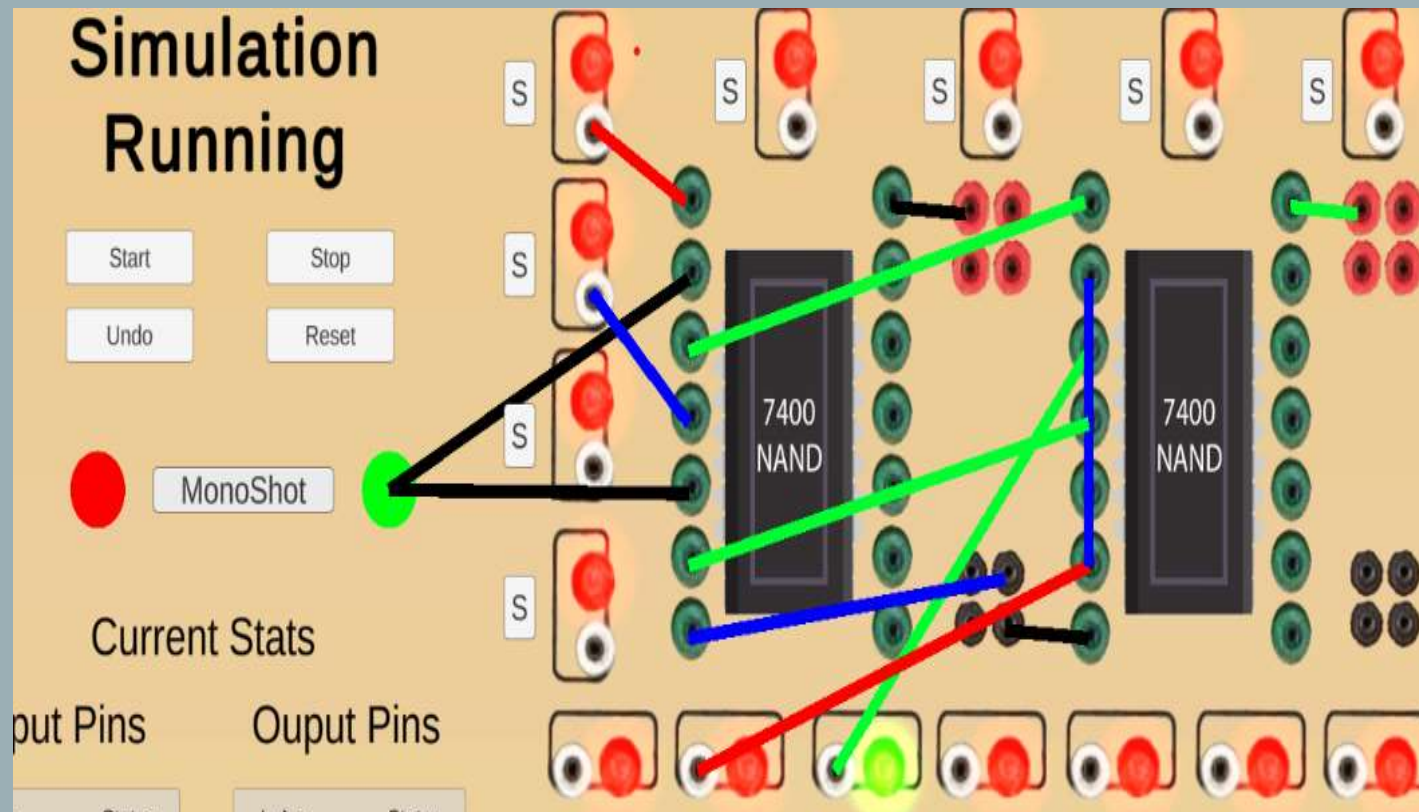


Video Reference - <https://youtu.be/bBxNEddS9hQ>

# *FLIP FLOP – D FLIP FLOP*

Clock	D	Q	Q'	Description
↓ » 0	X	Q	Q'	Memory no change
↑ » 1	0	0	1	Reset Q » 0
↑ » 1	1	1	0	Set Q » 1

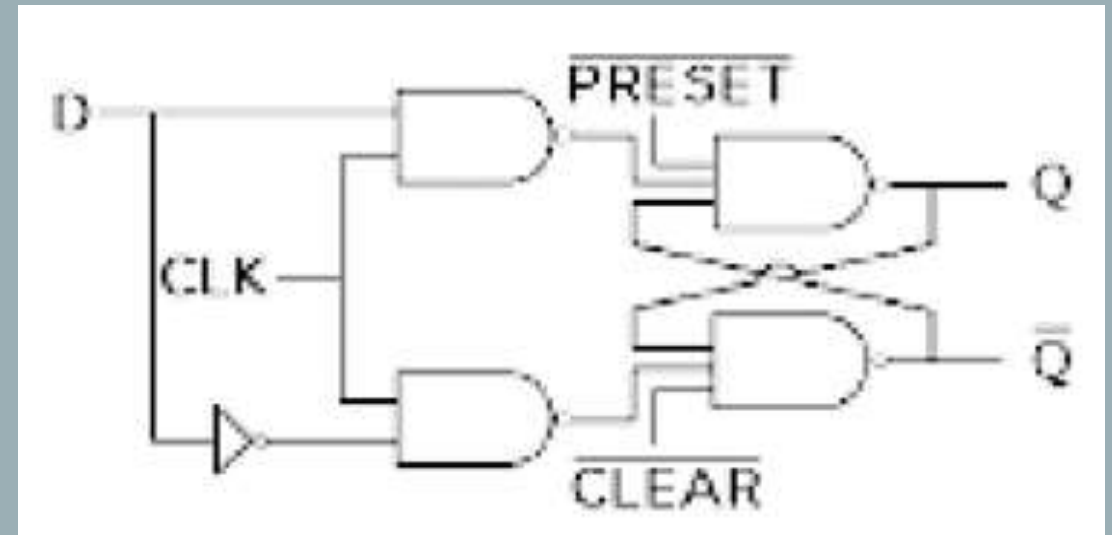

# *FLIP FLOP – D FLIP FLOP*

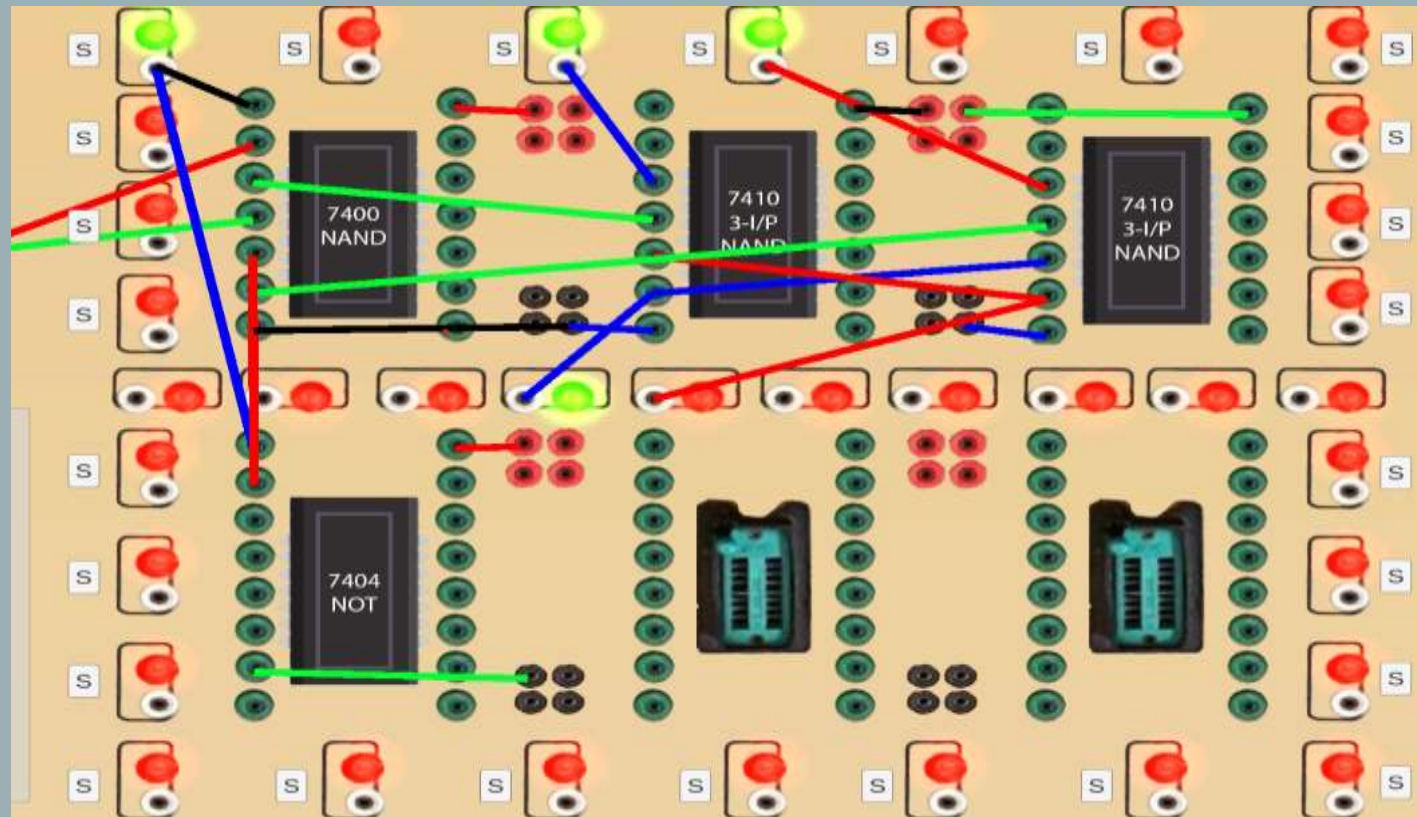

Video Reference - [https://youtu.be/GGVUtY\\_PyZY](https://youtu.be/GGVUtY_PyZY)






# ***FLIP FLOP – JK FLIP FLOP AND T FLIP FLOP***


- Flip-flops are digital circuits capable of storing binary states, used as memory elements in sequential logic circuits.
- A JK flip-flop is a sequential logic circuit capable of toggling its output based on its inputs and previous state.
- A T flip-flop is a digital circuit that toggles its output between two states based on its input and clock signal.

# *FLIP FLOP – JK FLIP FLOP*

Clock	J	K	$Q_{n+1}$	State
0	x	x	$Q_n$	
1	0	0	$Q_n$	Hold
1	0	1	0	Reset
1	1	1	1	Set
1	1	1	$\bar{Q}_n$	Toggle

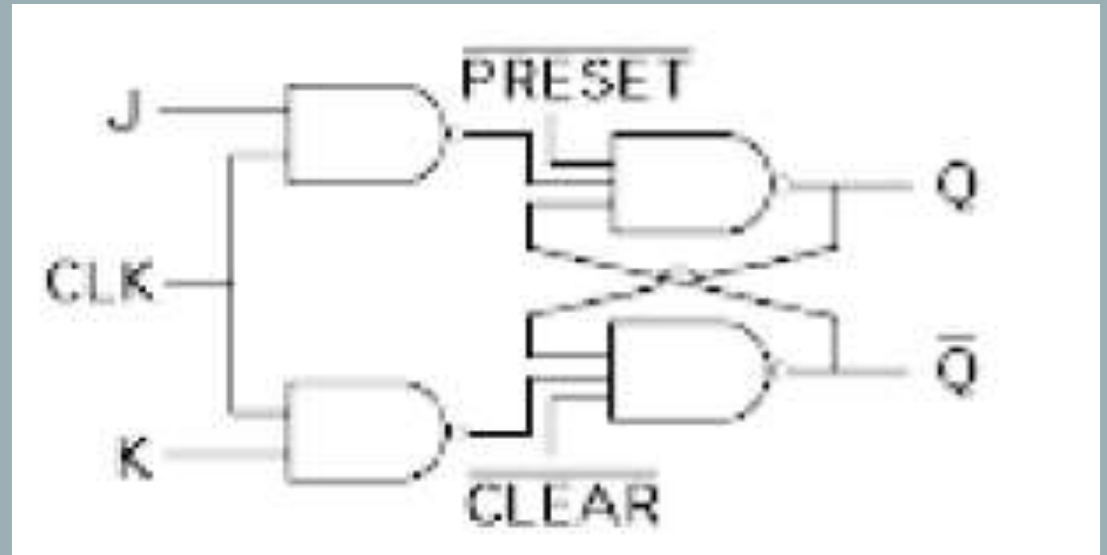


# *FLIP FLOP – JK FLIP FLOP*

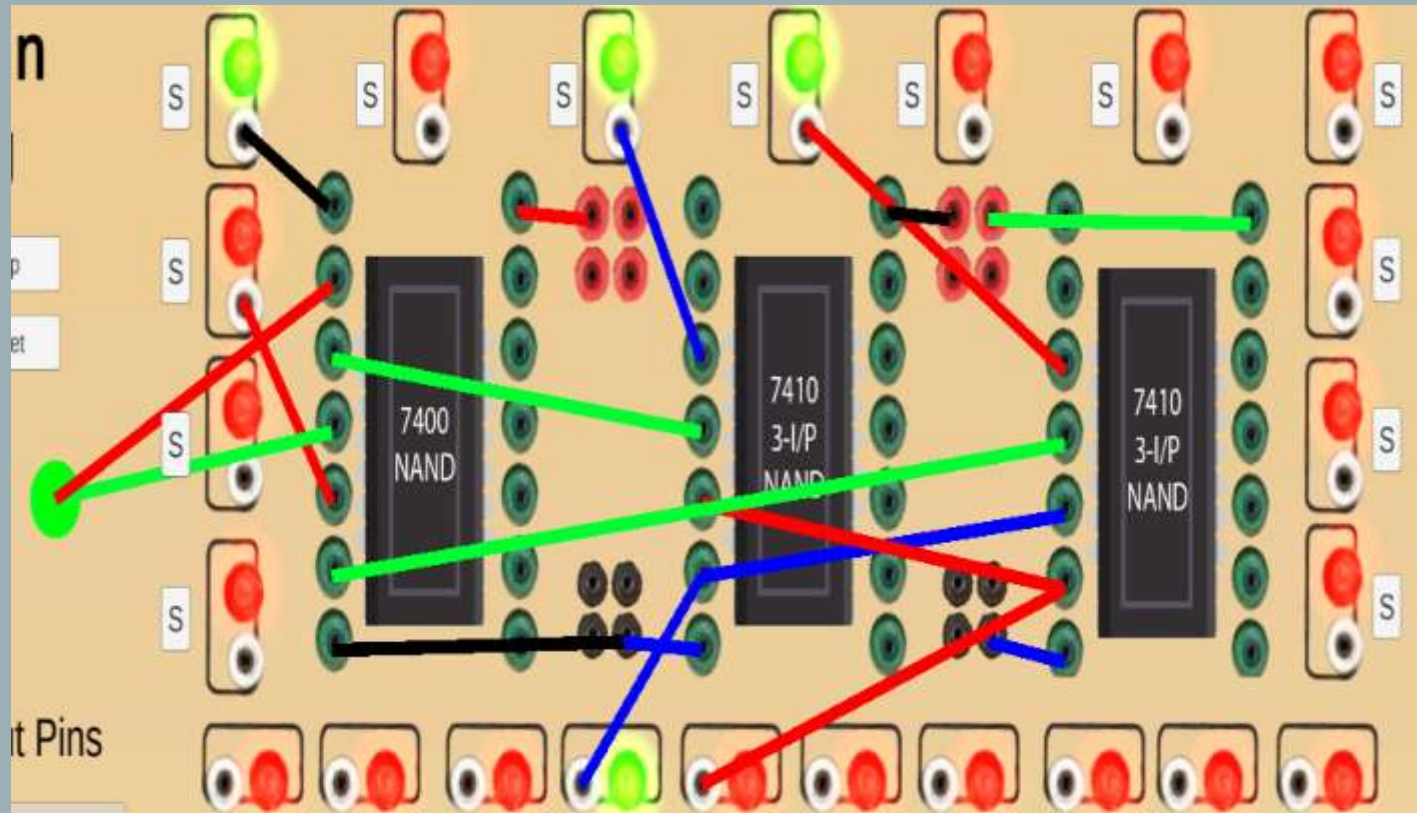

Video Reference - <https://youtu.be/nPQj0gH09RU>


# *FLIP FLOP – T FLIP FLOP*

	Previous		Next	
T	Q	Q'	Q	Q'
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

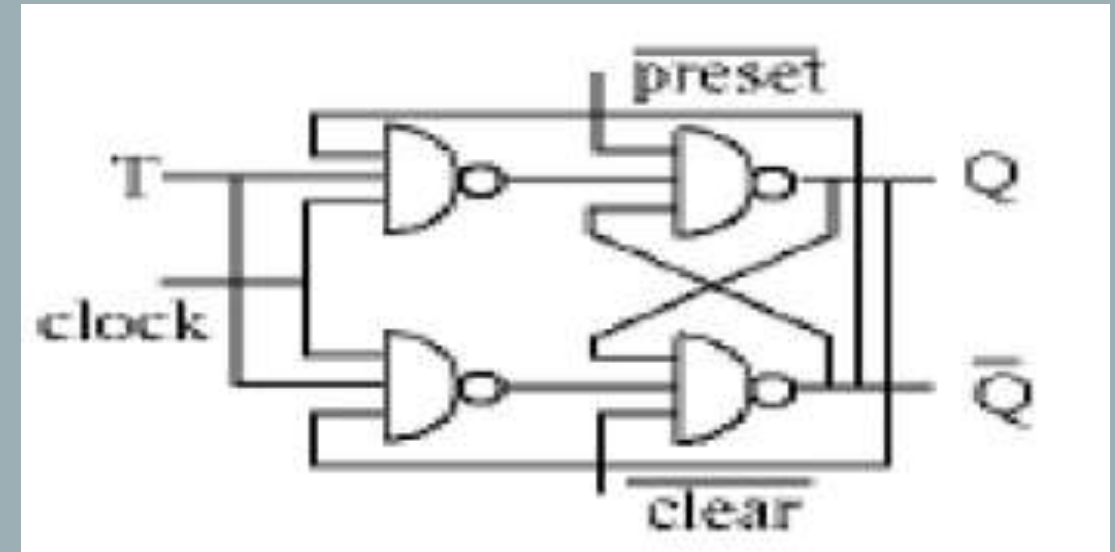



# *FLIP FLOP – T FLIP FLOP*

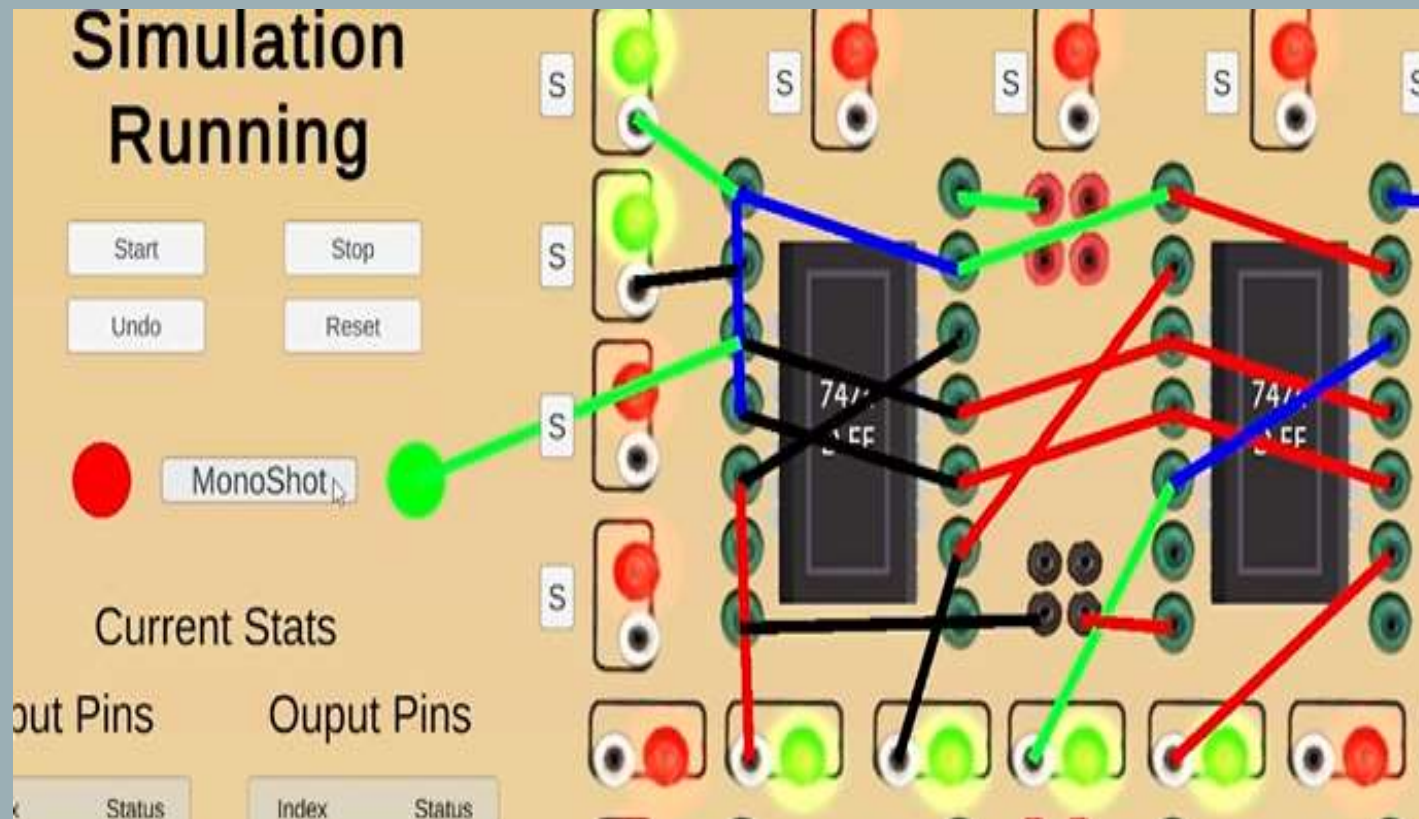

Video Reference - <https://youtu.be/Jn01ggVlMok>




# ***SHIFT REGISTERS***



- Shift registers are sequential digital circuits used to store and shift data serially or in parallel within electronic systems.
- SISO (Serial-In Serial-Out) shift register shifts data in and out serially, maintaining a single data stream.
- PISO (Parallel-In Serial-Out) shift register loads parallel data and outputs it serially, one bit at a time.

# *SHIFT REGISTER – SIS0 (IC 7474)*

Input (SI)	Clock Pulse	Shift Register				Serial Output (SO)
		Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	
0	↑	0	-	-	-	-
1	↑	1	0	-	-	-
1	↑	1	1	0	-	-
0	↑	0	1	1	0	0
1	↑	1	0	1	1	1
0	↑	0	1	0	1	1

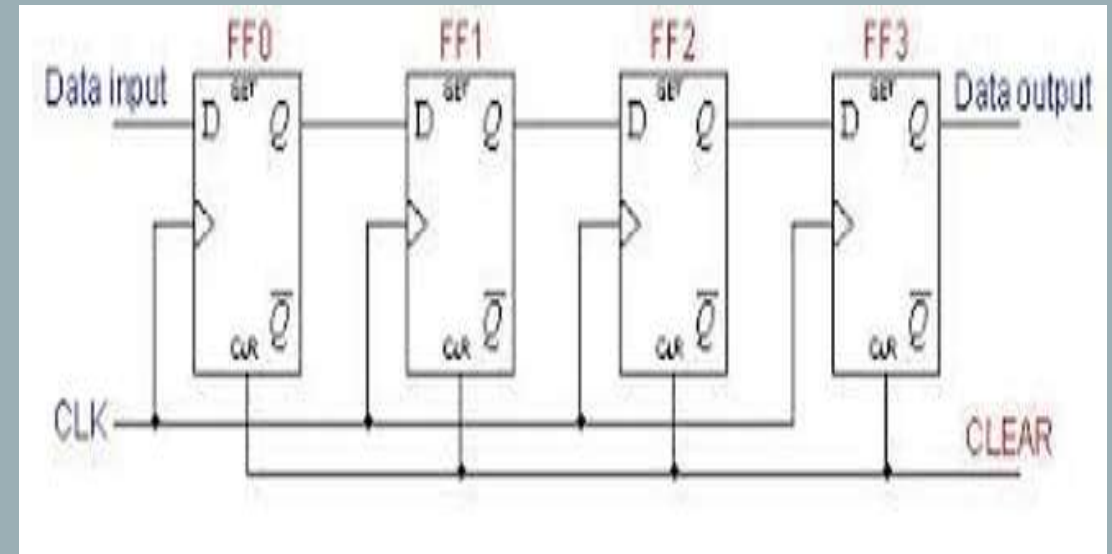

# *SHIFT REGISTER – SISO (IC 7474)*

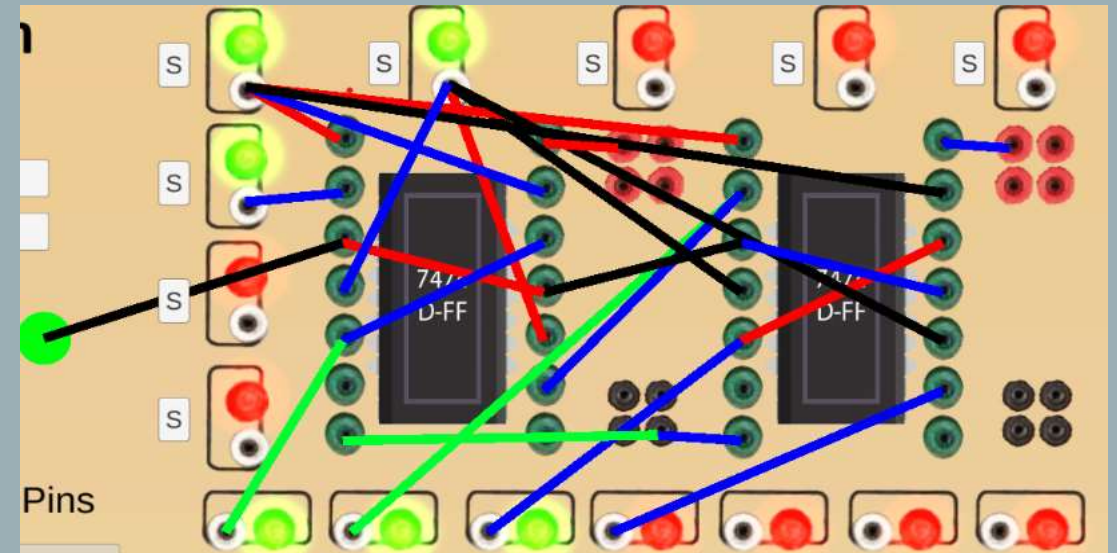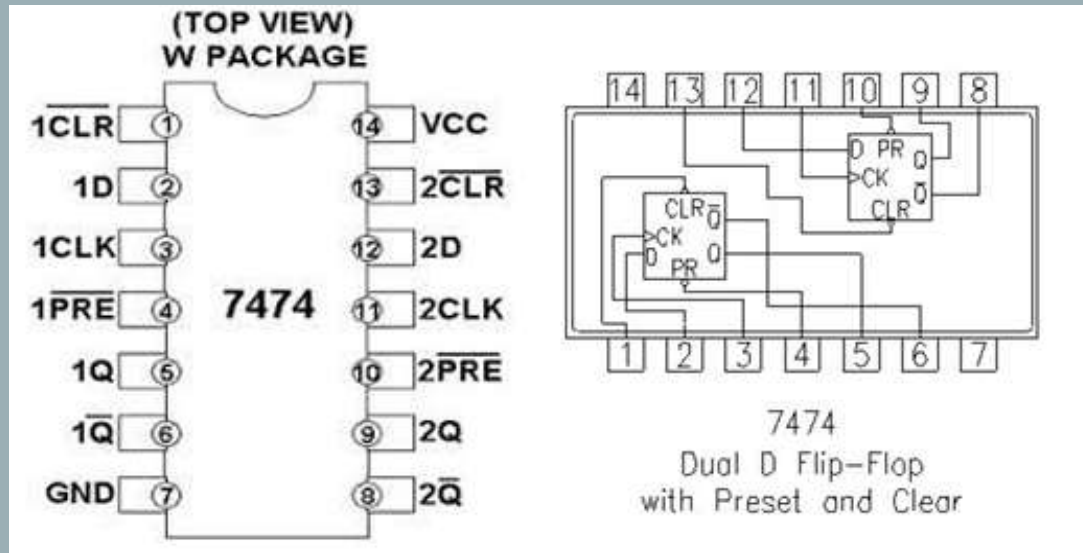


Video Reference - <https://youtu.be/yfyaXbC6rZ4>



# *SHIFT REGISTER – PISO*

Load/ (Shift)	Clock Pulse	Inputs				Serial Output (SO)
		D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	
1	↑	0	1	0	1	1
0	↑	0	0	1	0	0
0	↑	0	0	0	1	1
0	↑	0	0	0	0	0
1	↑	1	1	0	1	1

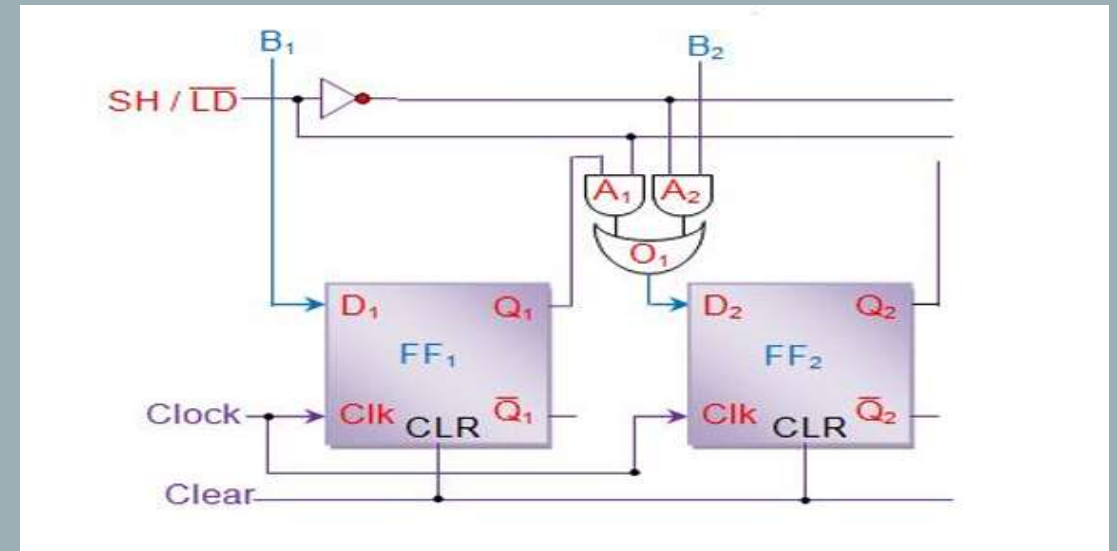











# ***RING COUNTER***

- Shift registers are sequential digital circuits used to store and shift data serially or in parallel within electronic systems.
- A Ring Counter is a type of shift register where the output of each stage is connected to the input of the next, creating a circular shifting pattern of binary values.

# RING COUNTER – IC 7495

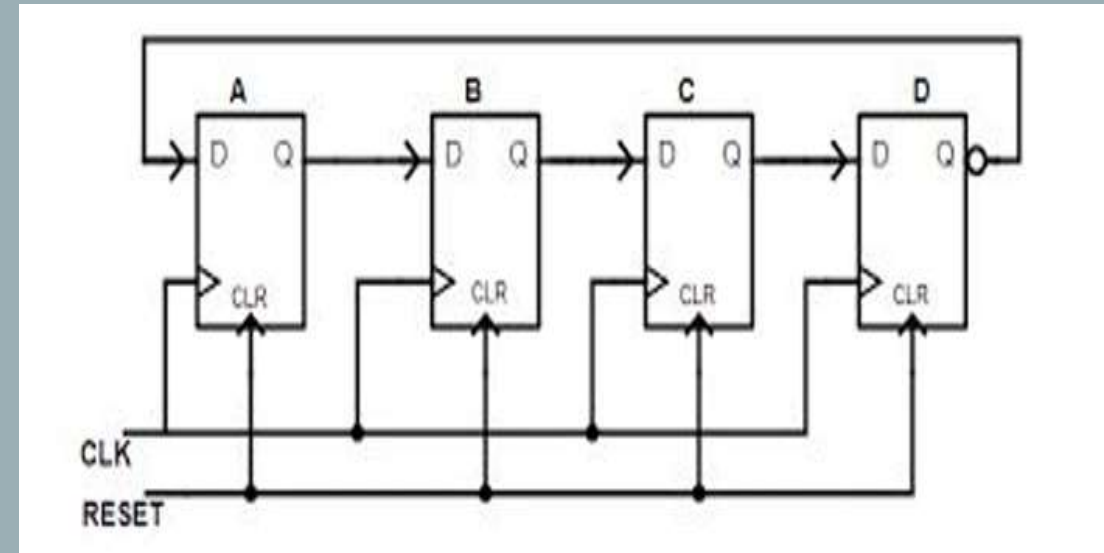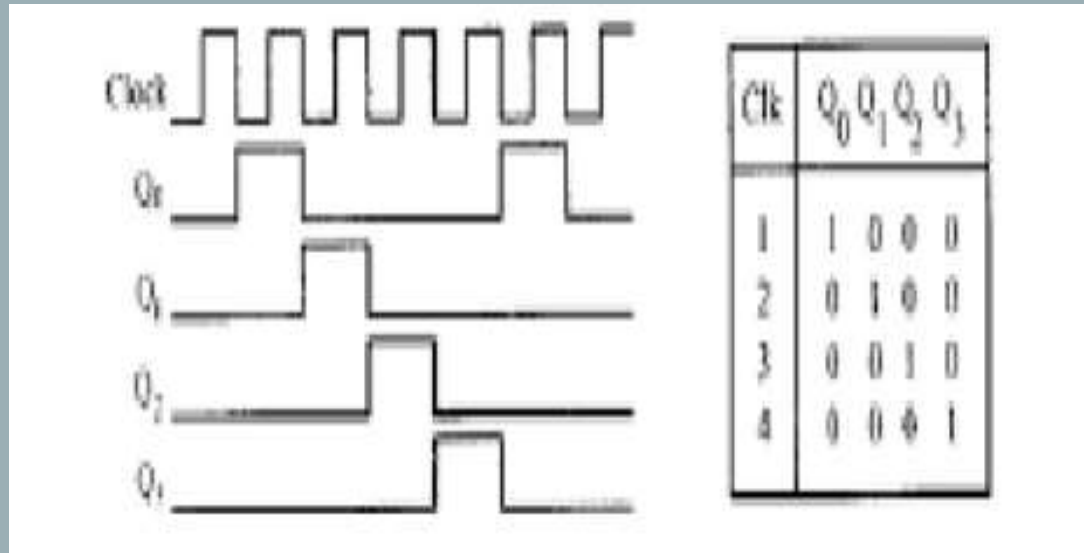

# RING COUNTER – IC 7495

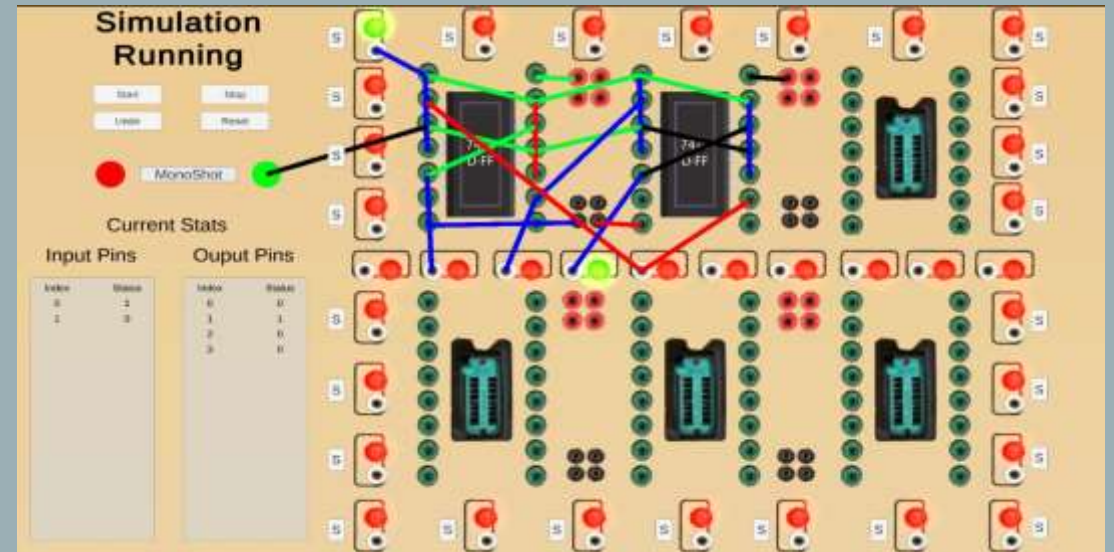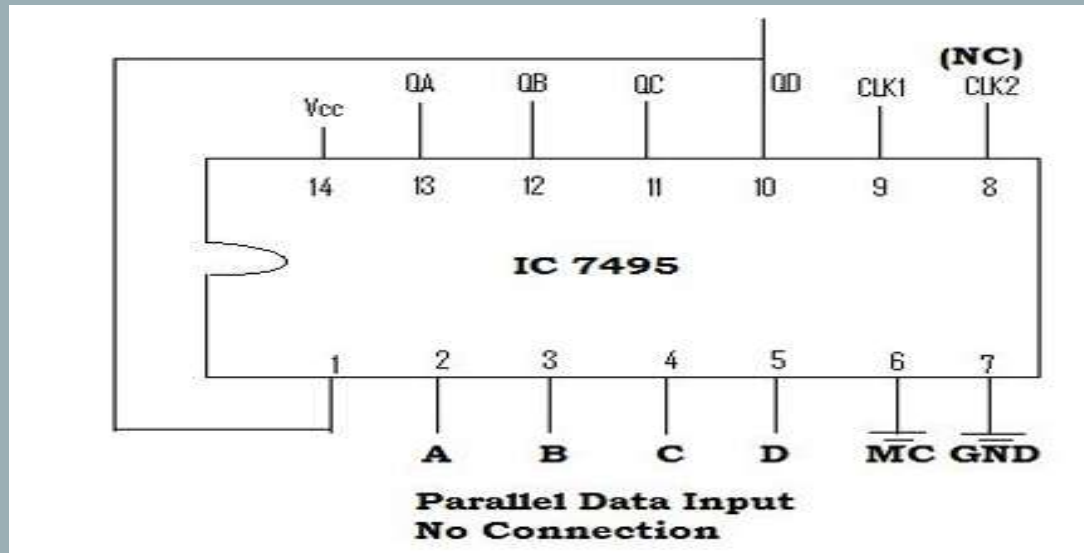

Video Reference - <https://youtu.be/Uiam6Edju4>




# ***JOHNSON COUNTER***


- Shift registers are sequential digital circuits used to store and shift data serially or in parallel within electronic systems.
- A Johnson counter, also known as a twisted-ring counter, is a type of shift register where the output of each stage is complemented and fed back to the input of the previous stage, resulting in a sequence of binary values with fewer states than a standard shift register.




# JOHNSON COUNTER

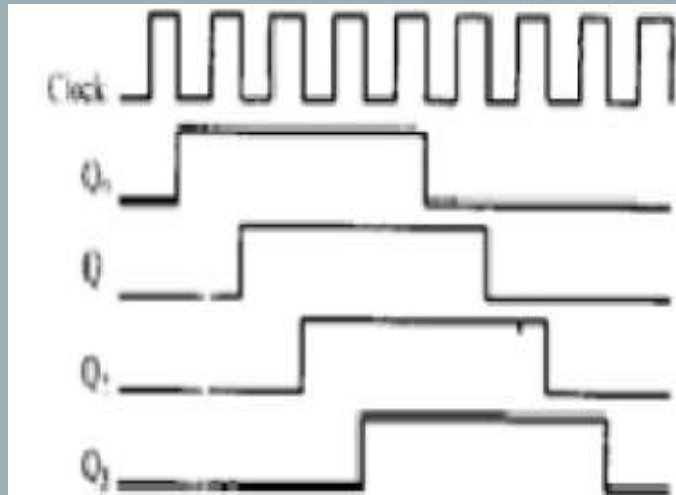

Clk	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

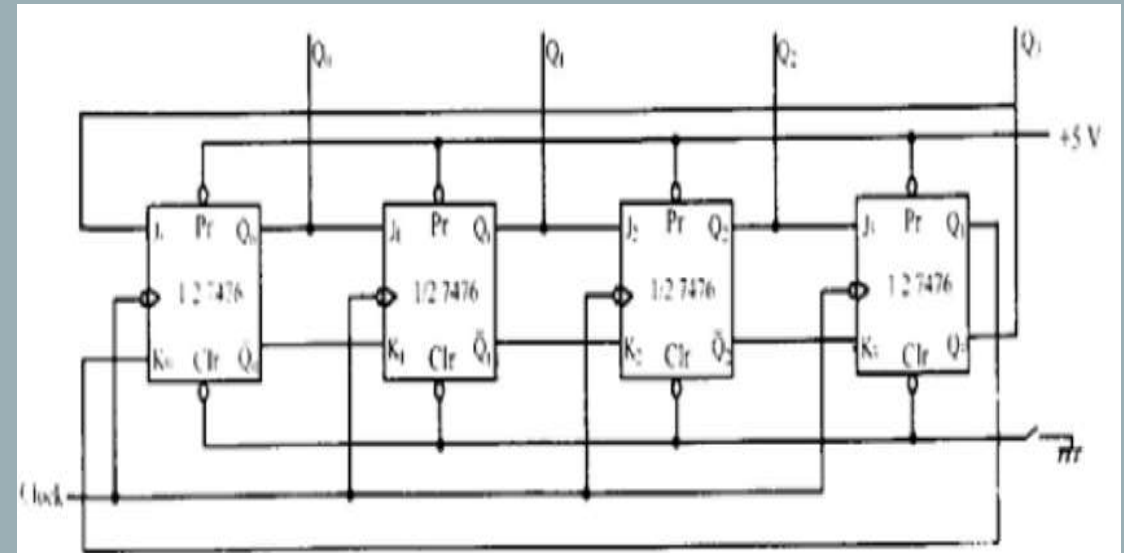

# *JOHNSON COUNTER*

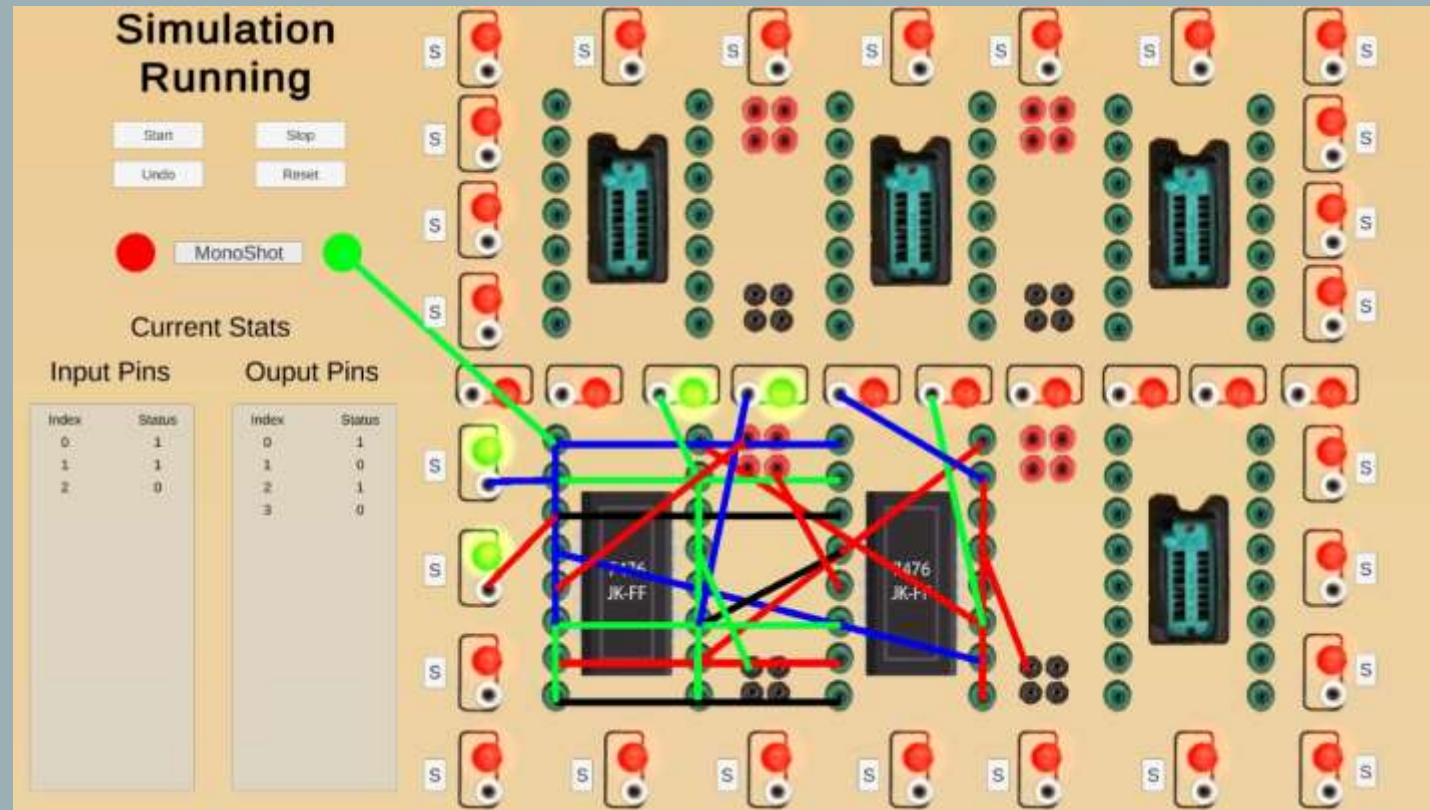

Video Reference - <https://youtu.be/OXQa5t9WyHk>




# ***ASYNCHRONOUS COUNTER***

- An asynchronous counter uses individual flip-flops triggered by their own clock signals, allowing each stage to change state independently.
- A mod 10 (decade) counter counts from 0 to 9 before resetting, commonly used in digital clocks and decimal applications.
- Mod 8, mod 5, and mod 7 counters count up to their respective modulus values before resetting, useful in various counting applications where specific sequence lengths are required. They can be implemented using Mod 10 Counter.





# *MOD 10/ DECADE COUNTER – IC 7490*

CLK	$Q_d$	$Q_c$	$Q_b$	$Q_a$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

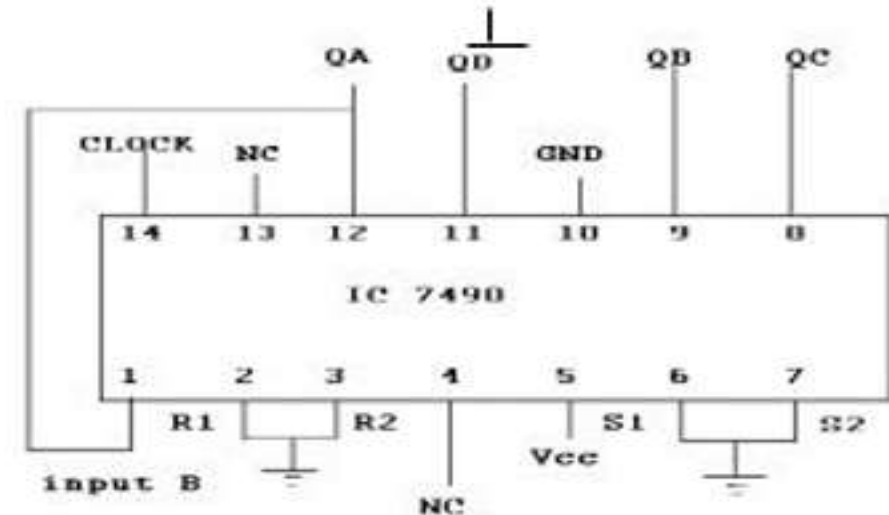

# MOD 10/ DECADE COUNTER – IC 7490

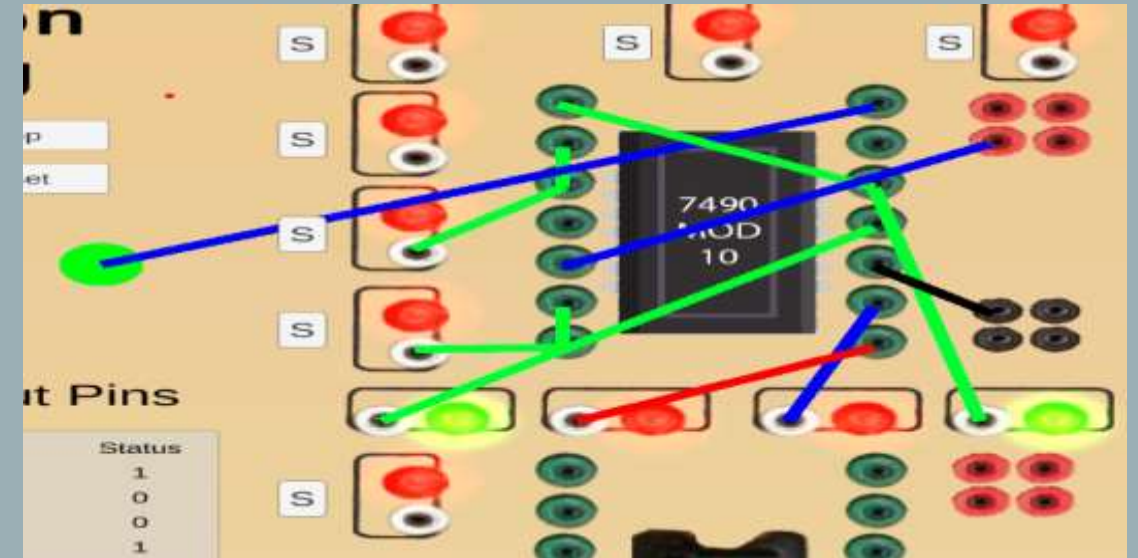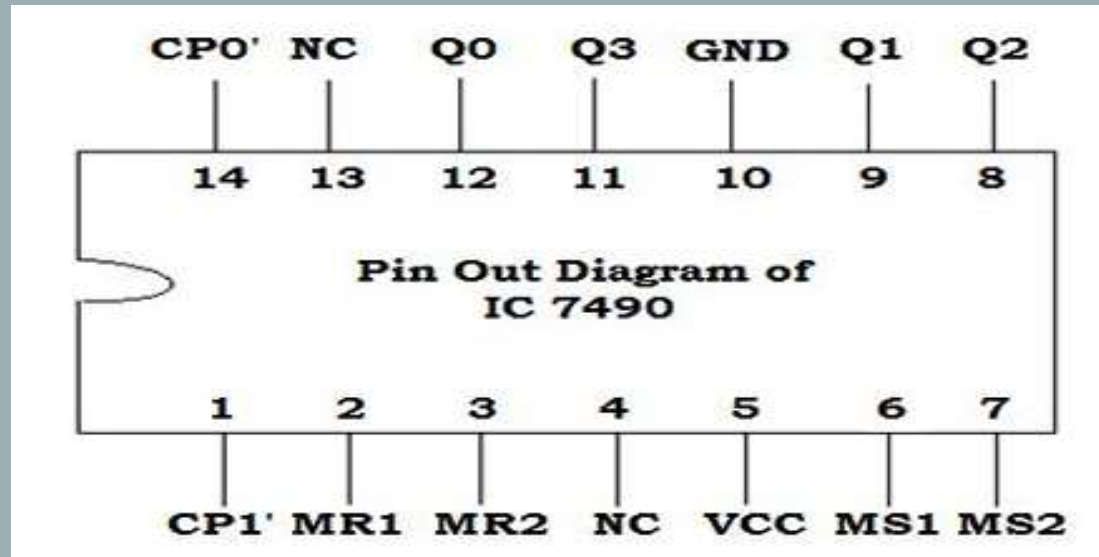


Video Reference - <https://youtu.be/rq-xwlMHTxw>






# *MOD 8 COUNTER*

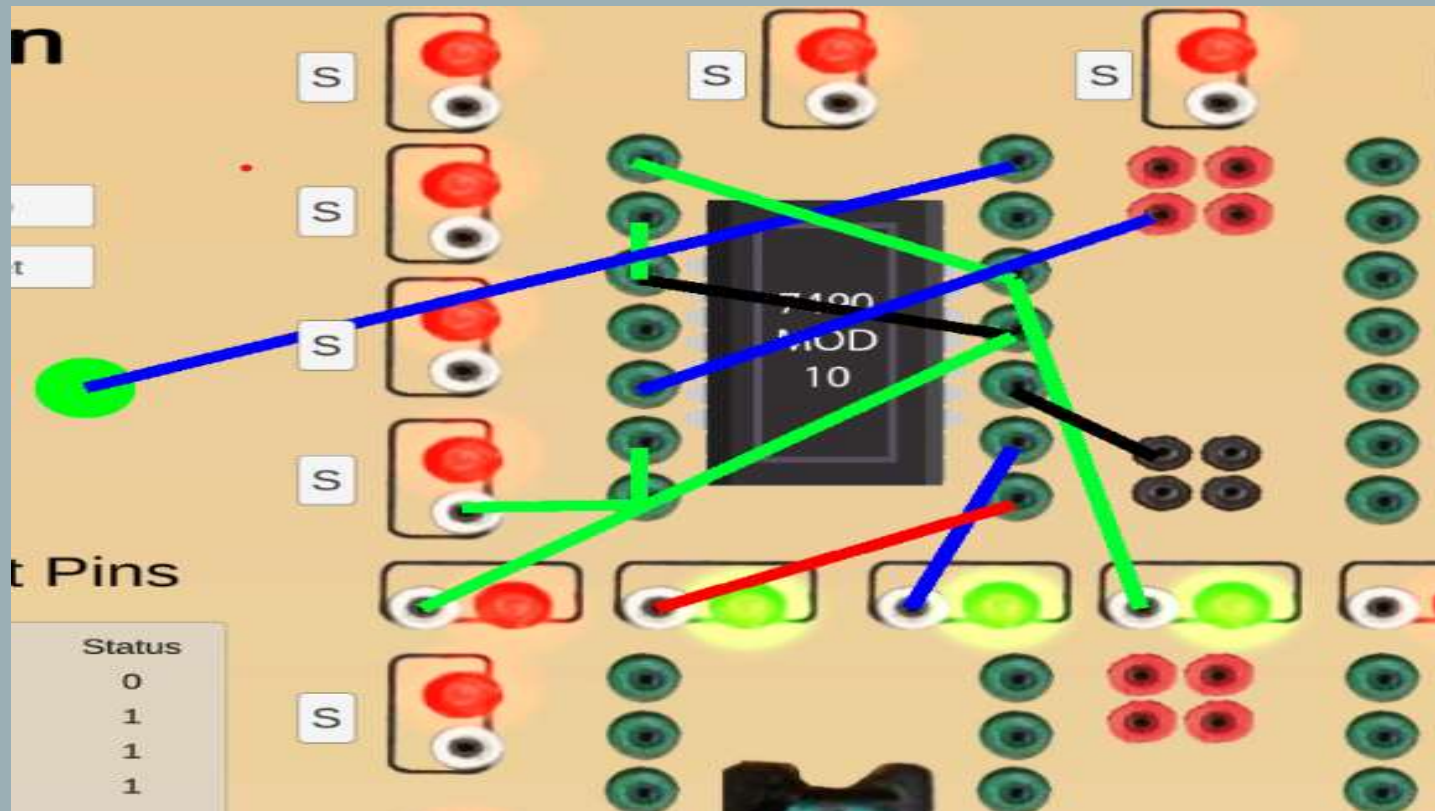


Video Reference - <https://youtu.be/SFdlqgU8Gn4>

# MOD 5 COUNTER

CLK	$Q_d$	$Q_c$	$Q_b$	$Q_a$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1

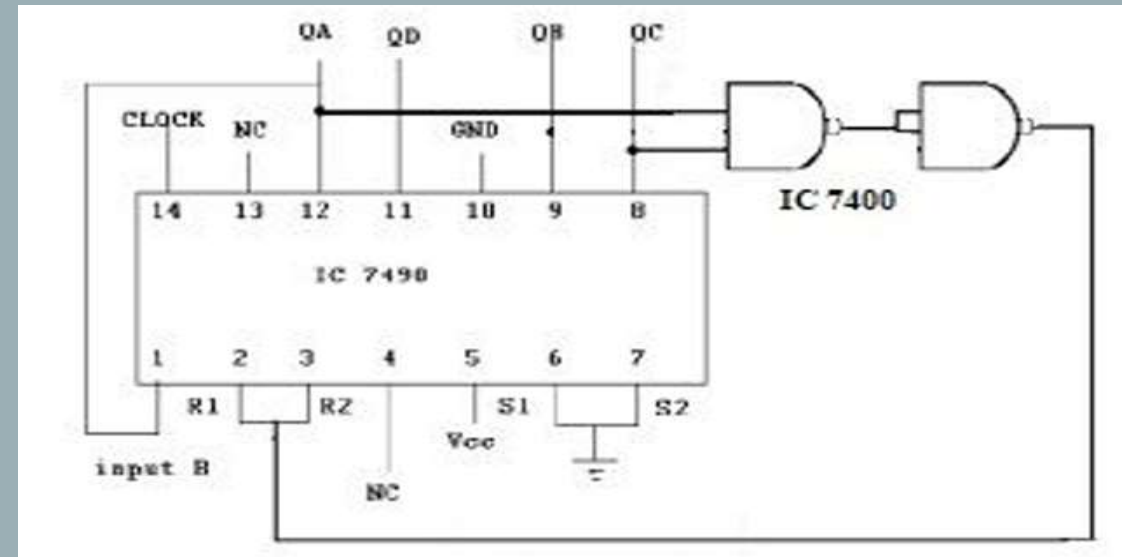

# *MOD 5 COUNTER*

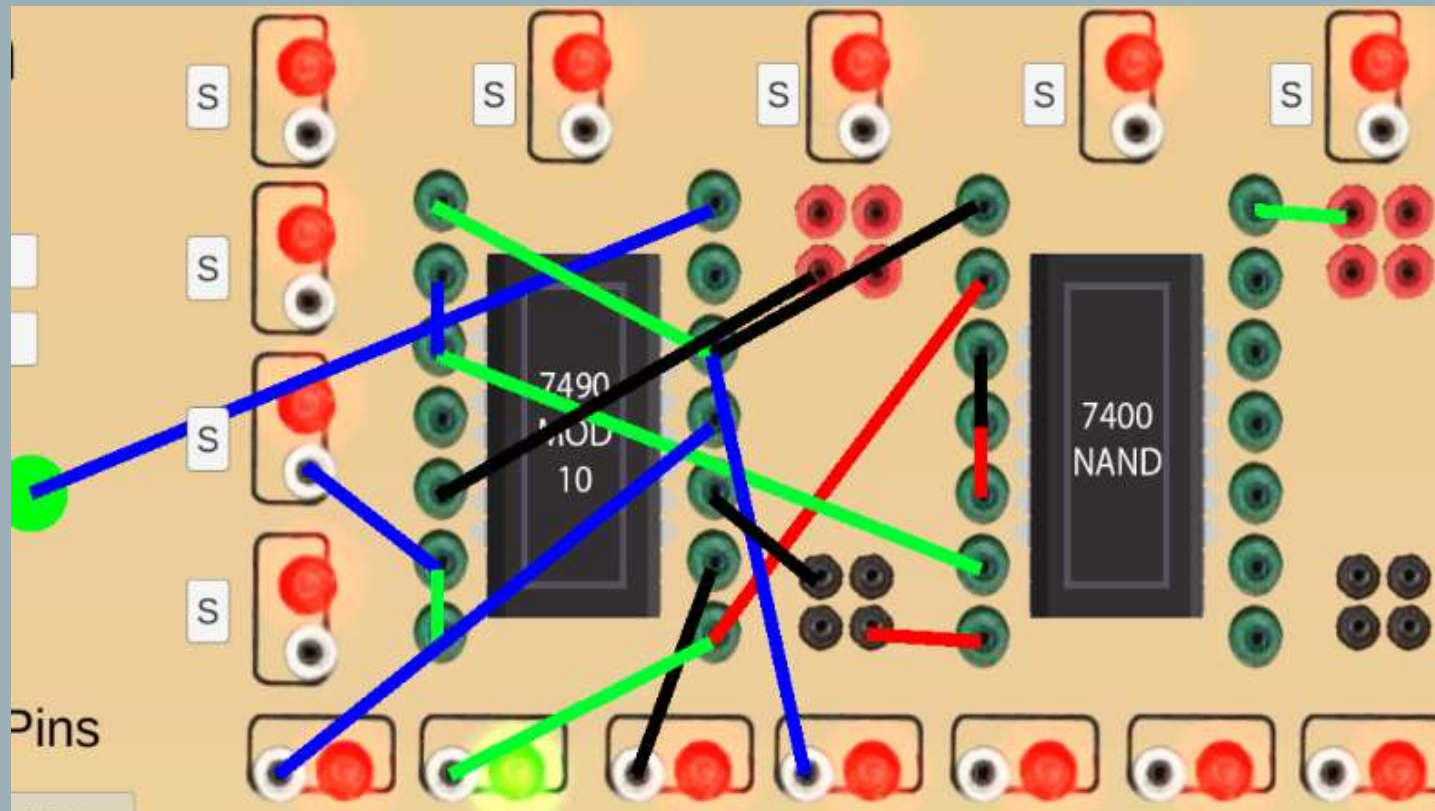


Video Reference - [https://youtu.be/vVb86u\\_AZhg](https://youtu.be/vVb86u_AZhg)



The diagram shows a 4-bit ripple-carry adder circuit. It consists of an IC 7490 (a decade counter) and two 7410 (NAND) gates. The IC 7490 has pins 14 (CLOCK), 13 (NC), 12 (QA), 11 (QD), 10 (QB), 9 (QC), 8 (B), 7 (S2), 6 (S1), 5 (Vcc), 4 (R2), 3 (R1), 2 (NC), and 1 (input B). The output B (pin 8) is connected to the input B (pin 1). The output QA (pin 12) is connected to the input of the first 7410 NAND gate. The output QD (pin 11) is connected to the input of the second 7410 NAND gate. The output QB (pin 10) is connected to the input of the first 7410 NAND gate. The output QC (pin 9) is connected to the input of the second 7410 NAND gate. The output of the first 7410 NAND gate is connected to the input of the second 7410 NAND gate. The output of the second 7410 NAND gate is connected to the input of the first 7410 NAND gate. The output of the first 7410 NAND gate is connected to the input of the second 7410 NAND gate. The output of the second 7410 NAND gate is connected to the input of the first 7410 NAND gate.



# *MOD 7 COUNTER*

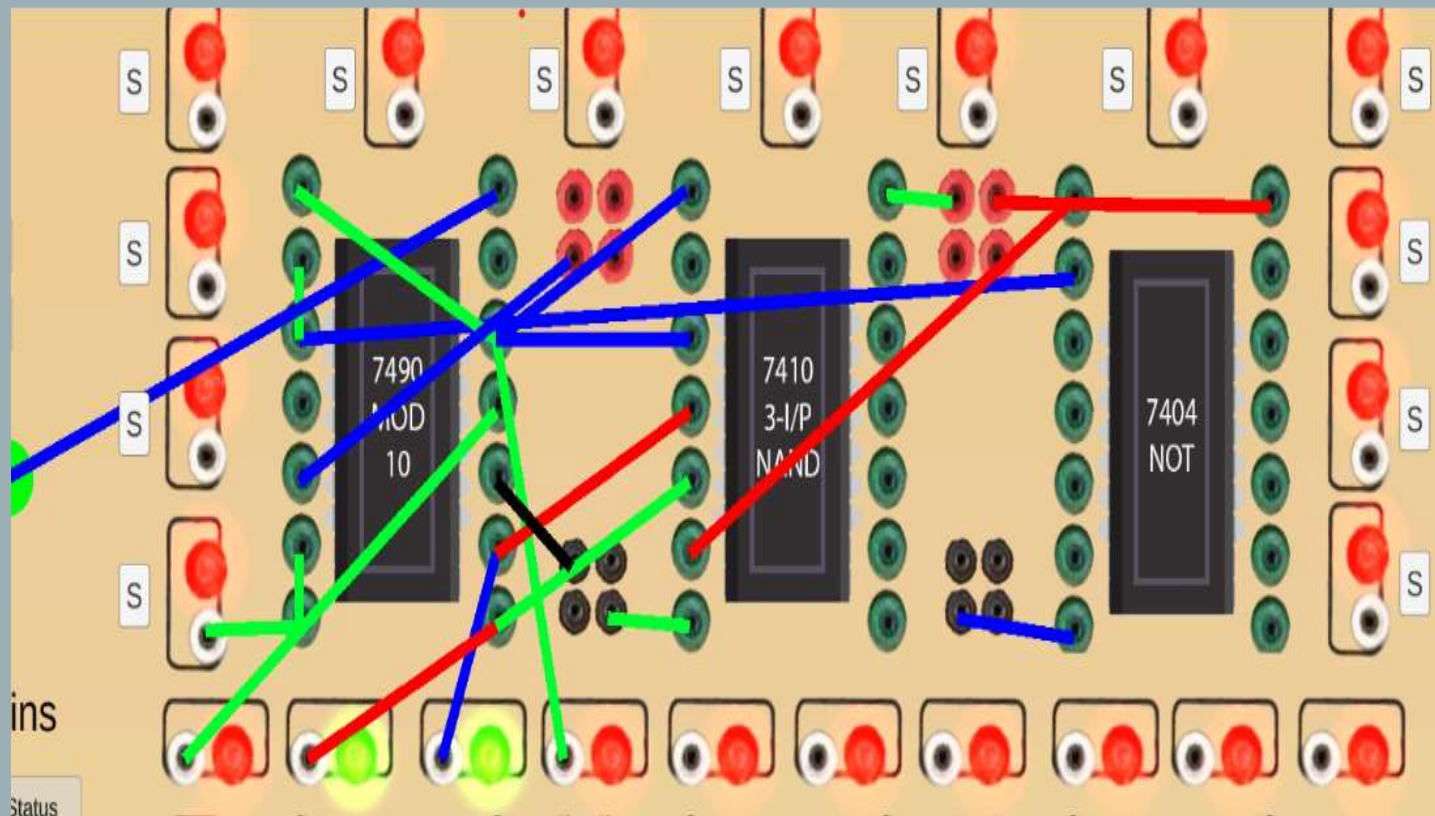

Video Reference - <https://youtu.be/ykBIbfEDYz4>



*Ready to Dive In?*  
*Simulation Starts*  
*Now!*